

PHYSICS • UPPER SIXTH

UPPER SIXTH — PHYSICS

CHAPTER 5

CAPACITORS

SUGGESTED TIME: 4 PERIODS

IN THIS CHAPTER

This chapter studies capacitors: how they store charge and energy in an electric field, how their capacitance depends on geometry and dielectric materials, and how they behave in series and parallel combinations. It ends with the time-dependent charging and discharging of capacitors through resistors, a cornerstone topic of the GCE Advanced Level Physics examination.

- By the end of this chapter I can define electric potential and potential difference and compute the work done in moving a charge in a uniform electric field.
- By the end of this chapter I can describe an electric dipole in a uniform field and calculate the torque acting on it.
- By the end of this chapter I can identify capacitors by their circuit symbols and physical appearance, and state the factors affecting capacitance.
- By the end of this chapter I can define capacitance, relative permittivity, and use $C = \epsilon_0 \epsilon_r A/d$ for a parallel-plate capacitor.
- By the end of this chapter I can measure capacitance experimentally using a charge-voltage method.
- By the end of this chapter I can derive and apply the equivalent capacitance of series and parallel combinations.



DOWNLOAD ON- BUCH

Free • Google Play
AI tutor, past papers,
results



GO ONBUCH+

All signed courses, unlimited AI
tutor, PDF sheets — OnBuch+
tab in the app

THIS SIGNED COURSE CONTAINS

COURSE

complete, illustrated,
step by step

METHODS

and worked examples

EXERCISES

exam style + solutions

SUMMARY SHEET

the essentials to
remember



Signed • OnBuch+

ONBUCH+ TEACHING TEAM
FOLLOWS THE OFFICIAL MINESEC SYLLABUS

OnBuch+

CONTENTS

1. Electric potential, work done and the electric dipole
2. Capacitors, capacitance and permittivity
3. Combinations of capacitors and energy stored
4. Charging and discharging through a resistor: the time constant
5. Integration activity
6. Methods and worked examples
7. Exercises
8. Solutions to the exercises
9. Summary sheet

CHAPTER OBJECTIVES

- By the end of this chapter I can define electric potential and potential difference and compute the work done in moving a charge in a uniform electric field.
- By the end of this chapter I can describe an electric dipole in a uniform field and calculate the torque acting on it.
- By the end of this chapter I can identify capacitors by their circuit symbols and physical appearance, and state the factors affecting capacitance.
- By the end of this chapter I can define capacitance, relative permittivity, and use $C = \epsilon_0 \epsilon_r A/d$ for a parallel-plate capacitor.
- By the end of this chapter I can measure capacitance experimentally using a charge-voltage method.
- By the end of this chapter I can derive and apply the equivalent capacitance of series and parallel combinations.
- By the end of this chapter I can calculate the charge and energy stored in any combination of capacitors connected to a d.c. supply.
- By the end of this chapter I can describe and sketch the charging and discharging of a capacitor through a resistor and define the time constant $\tau = RC$.
- By the end of this chapter I can use the exponential equations of charging and discharging and interpret them at $t = 0$ and as $t \rightarrow \infty$.

PREREQUISITES

- Electric charge, Coulomb's law and the concept of electric field (Lower Sixth, electrostatics)
- Uniform electric field between parallel plates, $E = V/d$ (Lower Sixth)
- Current, voltage, resistance and Ohm's law; simple d.c. circuits (Lower Sixth / O Level)
- Exponential and natural logarithm functions (Upper Sixth Mathematics)
- Work and energy concepts from mechanics (Lower Sixth)

1 ELECTRIC POTENTIAL, WORK DONE AND THE ELECTRIC DIPOLE

During the long dry-season evenings in Bamenda or Yaoundé, many families rely on rechargeable lamps and phone chargers that keep shining for a while even after the mains power from ENEO cuts off. Inside these devices, a component called a **capacitor** quietly stores electric energy and releases it when needed. The same principle explains why a camera flash can fire instantly, why a defibrillator can restart a heart, and why unplugging a television does not make its circuits safe to touch immediately. How much charge can such a device store, how fast does it fill up, and how quickly does it empty? This chapter answers these questions quantitatively.

Before we can describe how a capacitor stores energy, we need a precise way of talking about the energy per unit charge at a point in an electric field. That quantity is the **electric potential**. This first section therefore builds the essential vocabulary: potential, potential difference, the work done in moving a charge, and the behaviour of an electric dipole in a field.

1.1 Electric potential at a point

Intuition. Imagine a hilly landscape. A ball placed on a slope "wants" to roll downhill: the height tells you how much gravitational energy each kilogram of the ball possesses. In the same way, an electric field is a kind of invisible landscape for charges. A positive charge placed in the field "wants" to move in a certain direction, and the electric potential tells you how much electrical energy each coulomb of charge possesses at that point. Just as we measure height relative to sea level, we measure potential relative to a reference point, chosen to be infinity, where the potential is taken as zero.

DEFINITION Electric potential

The **electric potential** V at a point in an electric field is the work done per unit positive charge in bringing a small positive test charge from infinity to that point, without accelerating it and without disturbing the field:

$$V = \frac{W_{\infty \rightarrow P}}{q}.$$

The SI unit of potential is the **volt** (V): $1\text{ V} = 1\text{ J C}^{-1}$. Potential is a scalar quantity.

DEFINITION Potential difference

The **potential difference** (p.d.) between two points A and B is the work done per unit positive charge in moving a charge from A to B :

$$V_{AB} = V_B - V_A = \frac{W_{A \rightarrow B}}{q}.$$

It is also measured in volts. In practice, all circuit measurements are potential differences;

a voltmeter connected between two points reads V_{AB} .

WARNING Infinity is just a reference

Saying "the potential at P is $+50\text{ V}$ " means: it takes 50 J of work per coulomb to bring a positive charge from infinity to P (against the field of a positive source charge, for example). Only potential differences have physical consequences; the choice of zero is a convention, exactly like choosing sea level for altitudes.

DID YOU KNOW? Potential in Cameroon's high-voltage lines

The high-voltage transmission lines you see crossing the countryside (e.g., from Song Loulou to Yaoundé) operate at potentials of 225 kV or 90 kV relative to earth. This high potential reduces the current for a given power, minimising I^2R losses over hundreds of kilometres. The "potential" of the line is always a potential difference with respect to the ground.

1.2 Work done in moving a charge: $W = qV$

From the definition above, the work done in moving a charge q through a potential difference V follows immediately.

PROPERTY Work done and potential difference

When a charge q moves from a point A to a point B between which the p.d. is $V = V_B - V_A$, the work done by the electric field is

$$W_{\text{field}} = q(V_A - V_B) = -qV,$$

while the work that must be supplied by an external agent to move the charge slowly (without change of kinetic energy) is

$$W_{\text{ext}} = q(V_B - V_A) = qV.$$

A positive charge released freely in a field accelerates from high potential to low potential, converting electrical potential energy into kinetic energy. A negative charge does the opposite.

WARNING Work done BY the field versus BY an external agent

This is the most frequent source of sign errors at the GCE. Ask yourself: who is doing the work?

- If the field pushes the charge (charge moving the way the field "wants" it to go), the work done by the field is positive and the charge speeds up.
- If you push the charge against the field, the work done by you (the external agent) is positive, and the work done by the field is negative.

Always write down which work you are computing before substituting signs for q and V .

EXAMPLE Moving a charge between two points

A charge $q = +2.0 \text{ } \mu\text{C}$ is moved slowly from a point A where $V_A = 100 \text{ V}$ to a point B where $V_B = 250 \text{ V}$. The p.d. is $V = V_B - V_A = 150 \text{ V}$. The external agent must supply

$$W_{\text{ext}} = qV = 2.0 \times 10^{-6} \times 150 = 3.0 \times 10^{-4} \text{ J},$$

while the field does work $W_{\text{field}} = -3.0 \times 10^{-4} \text{ J}$ (it opposes the motion, since a positive charge is being pushed towards higher potential).

1.3 Field and potential: $E = V/d$ in a uniform field

Consider two large parallel metal plates separated by a distance d , one at potential V and the other at potential 0. Between them the field is **uniform**: the field lines are parallel and equally spaced. Move a charge q from the low-potential plate to the high-potential plate, a distance d against the field. The external force needed is $F = qE$ (constant, since E is uniform), so the work supplied is

$$W_{\text{ext}} = Fd = qEd.$$

But by definition this same work equals qV . Hence $qEd = qV$, which gives the key result.

PROPERTY Relation between field and potential in a uniform field


Between two points separated by a distance d measured along the field direction in a uniform field,

$$E = \frac{V}{d}$$


The electric field points from high potential to low potential. This relation gives an alternative SI unit for E : the volt per metre, V m^{-1} , which is identical to N C^{-1} .

More generally, the field is related to how rapidly the potential changes with position: $E = -\frac{dV}{dx}$.

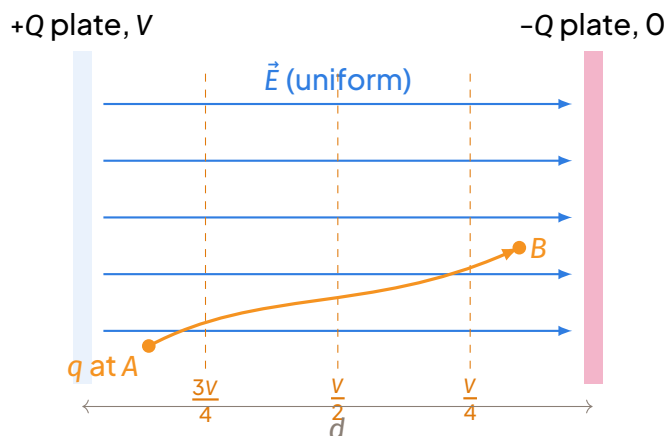The minus sign says the field points in the direction of decreasing potential, just as a ball rolls downhill.



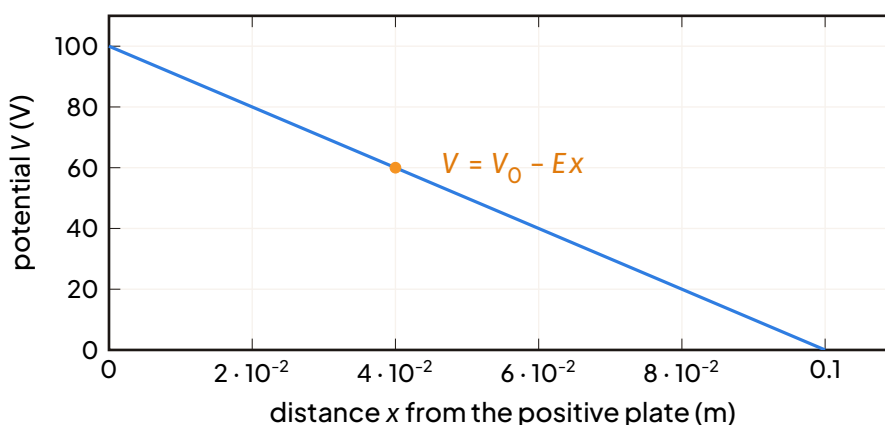Uniform field between parallel plates. Solid arrows: field lines (high to low potential). Dashed lines: equipotentials, everywhere perpendicular to the field. The work done on charge q depends only on the potentials at A and B, not on the path taken.



Potential versus position between parallel plates ($V_0 = 100 \text{ V}$, $d = 0.10 \text{ m}$, so $E = 1000 \text{ V m}^{-1}$). The potential falls linearly; the magnitude of the gradient is the field strength.

EXPERIMENT Mapping equipotentials (laboratory)

Apparatus: Conductive paper (teledeltos), power supply (0–12 V), two metal electrodes (bars or points), voltmeter, connecting wires. Procedure:

1. Place the conductive paper on a flat board. Fix the two electrodes on the paper and connect them to the power supply.

2. Set the p.d. between electrodes to about 6 V.
3. Use the voltmeter probe (negative lead fixed on one electrode) to find points on the paper where the reading is 1 V, 2 V, 3 V, etc. Mark these points.
4. Join points of equal potential to draw equipotential lines. Draw field lines perpendicular to them.

Observation: For parallel bar electrodes, equipotentials are straight, parallel, equally spaced lines (uniform field). For point electrodes, they are curved, spacing increases with distance (radial field).

KEY POINTS Equipotential surfaces

An **equipotential surface** is a surface on which the potential is the same everywhere.

- No work is done in moving a charge along an equipotential ($W = q\Delta V = 0$).
- Field lines always cross equipotentials at right angles.
- Between parallel plates, the equipotentials are planes parallel to the plates and equally spaced (uniform field).
- Around a point charge, the equipotentials are concentric spheres, getting farther apart as the field weakens.

1.4 Kinetic energy gained by an accelerated charge

When a charge is free to move, energy conservation replaces the external agent: the electrical potential energy lost becomes kinetic energy. This is the working principle of the **electron gun** inside old television tubes, oscilloscopes and X-ray tubes, and it reappears constantly in later chapters (motion of charges in fields, particle accelerators).

METHOD Solving acceleration-of-charge problems with $\frac{1}{2}mv^2 = qV$

1. Identify the charge q (magnitude and sign) and the p.d. V through which it is accelerated. Use the magnitude of the p.d. that causes the speed-up.
2. State energy conservation: loss of electrical potential energy = gain of kinetic energy:

$$\frac{1}{2}mv^2 - \frac{1}{2}mv_0^2 = |q|V.$$

If the particle starts from rest, $v_0 = 0$.

3. Solve for the unknown: $v = \sqrt{\frac{2|q|V}{m}}$.

4. Check: every numerical answer must carry its SI unit and sensible significant figures.

WORKED EXAMPLE 1 Electron accelerated through 2.0 kV

An electron (charge $e = 1.60 \times 10^{-19}$ C, mass $m_e = 9.11 \times 10^{-31}$ kg) is emitted from rest at the cathode of an electron gun and accelerated through a p.d. of 2.0 kV. Calculate (a) the kinetic energy gained, in joules and in electronvolts; (b) the final speed of the electron.

SOLUTION

(a) The electron, being negative, is accelerated from low to high potential; the magnitude of the p.d. is $V = 2.0 \times 10^3$ V. Energy conservation gives

$$E_k = eV = 1.60 \times 10^{-19} \times 2.0 \times 10^3 = 3.2 \times 10^{-16} \text{ J.}$$

By definition of the **electronvolt** ($1 \text{ eV} = e \times 1 \text{ V} = 1.60 \times 10^{-19} \text{ J}$), this is simply $E_k = 2.0 \text{ keV}$.

(b) Since the electron starts from rest,

$$\frac{1}{2} m_e v^2 = eV \quad \Rightarrow \quad v = \sqrt{\frac{2eV}{m_e}} = \sqrt{\frac{2 \times 3.2 \times 10^{-16}}{9.11 \times 10^{-31}}}.$$

$$v = \sqrt{7.03 \times 10^{14}} = 2.7 \times 10^7 \text{ m s}^{-1}.$$

This is about 9% of the speed of light: electron guns produce genuinely fast particles from modest voltages.

1.5 The electric dipole

Many molecules, such as water, are electrically neutral overall yet behave as if a small positive charge and a small negative charge sit at slightly different positions. Such a system is an **electric dipole**, and understanding it explains why charged objects attract neutral pieces of paper and why some liquids rotate the direction of an applied field.

DEFINITION Electric dipole and dipole moment

An **electric dipole** consists of two equal and opposite point charges $+q$ and $-q$ separated by a fixed distance $2a$ (the separation). Its **electric dipole moment** is the vector

$$\vec{p} = q \vec{d}, \quad p = q \times (\text{separation}) = 2aq,$$

directed from the negative charge to the positive charge. The SI unit of p is the coulomb-metre (C m).

1.6 Torque on a dipole in a uniform field

Place the dipole in a uniform field $\vec{E}$, with its axis making an angle θ with the field. The force on $+q$ is $\vec{F}_+ = q\vec{E}$ (along the field) and the force on $-q$ is $\vec{F}_- = -q\vec{E}$ (opposite the field). The two forces are equal, opposite and parallel but act at different points: they form a **couple**. The net force is zero (the dipole does not translate), but there is a net **torque**.

Taking moments about the centre of the dipole: each force has magnitude qE and lever arm $a \sin \theta$, and both moments act in the same sense of rotation, so

$$\tau = 2 \times qE a \sin \theta = (2aq)E \sin \theta.$$


PROPERTY Torque on an electric dipole — proof examinable

A dipole of moment p placed at an angle θ to a uniform field E experiences a torque

$$\tau = pE \sin \theta$$

which tends to align the dipole with the field. In vector form, $\vec{\tau} = \vec{p} \times \vec{E}$.

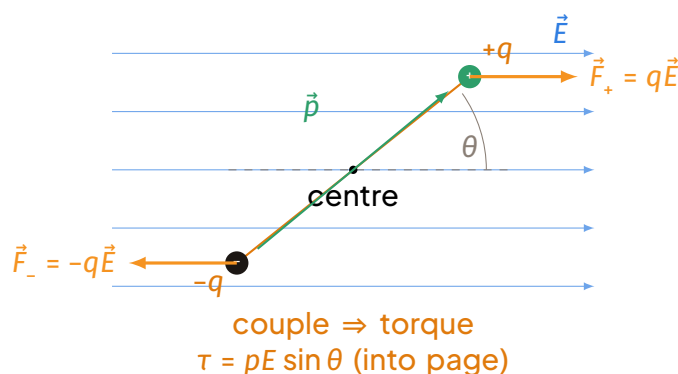- $\theta = 0$ (dipole parallel to $\vec{E}$): $\tau = 0$, stable equilibrium. A small displacement produces a restoring torque.
- $\theta = 180^\circ$ (dipole antiparallel): $\tau = 0$, unstable equilibrium. The slightest disturbance flips the dipole round.
- $\theta = 90^\circ$: maximum torque, $\tau_{\max} = pE$.



A dipole at angle θ in a uniform field. The forces $q\vec{E}$ and $-q\vec{E}$ form a couple: zero net force, but a torque $\tau = pE \sin \theta$ that rotates the dipole towards alignment with $\vec{E}$.

WORKED EXAMPLE 2 Torque on a water-like dipole

A molecule is modelled as a dipole with charges $\pm 1.0 \times 10^{-20}$ C separated by 4.0×10^{-10} m. It sits in a uniform field $E = 5.0 \times 10^5$ V m $^{-1}$ making an angle of 30° with the field. Find (a) the

dipole moment; (b) the torque on the molecule; (c) the maximum possible torque.

SOLUTION

(a) $p = q \times \text{separation} = 1.0 \times 10^{-20} \times 4.0 \times 10^{-10} = 4.0 \times 10^{-30} \text{ C m}.$

(b) $\tau = pE \sin \theta = 4.0 \times 10^{-30} \times 5.0 \times 10^5 \times \sin 30^\circ = 1.0 \times 10^{-24} \text{ N m}.$

(c) $\tau_{\text{max}} = pE = 2.0 \times 10^{-24} \text{ N m}, \text{ occurring at } \theta = 90^\circ.$

Extension — work done in rotating a dipole. To rotate a dipole slowly from alignment ($\theta = 0$) to an angle θ , an external agent must work against the restoring torque. The work required is

$$W = \int_0^\theta pE \sin \theta' d\theta' = pE(1 - \cos \theta),$$

so the dipole has its lowest potential energy when aligned with the field (stable equilibrium) and its highest when antiparallel. This explains why polar molecules in a liquid align with an applied field, an idea we shall meet again when we study dielectrics inside capacitors. (This integral treatment is an extension: at GCE level, only the qualitative conclusion is required.)

EXERCISE 1 Practice

- Two parallel plates are 5.0 mm apart and the p.d. between them is 200 V. Calculate the electric field strength between the plates.
- A proton ($q = +e$, $m = 1.67 \times 10^{-27} \text{ kg}$) is accelerated from rest through 5.0 kV. Find its final kinetic energy and speed.
- A dipole of moment $2.0 \times 10^{-29} \text{ C m}$ lies in a field of $1.0 \times 10^6 \text{ V m}^{-1}$. At what angle is the torque half its maximum value?

SOLUTION Exercise 1

1. $E = V/d = 200/(5.0 \times 10^{-3}) = 4.0 \times 10^4 \text{ V m}^{-1}.$

2. $E_k = eV = 1.60 \times 10^{-19} \times 5.0 \times 10^3 = 8.0 \times 10^{-16} \text{ J}; \text{ then } v = \sqrt{2E_k/m} = \sqrt{1.6 \times 10^{-15}/1.67 \times 10^{-27}} = 9.8 \times 10^5 \text{ m s}^{-1}.$

3. $\tau_{\text{max}} = pE$, and $\tau = pE \sin \theta = \frac{1}{2}pE$ gives $\sin \theta = 0.5$, so $\theta = 30^\circ$ (or 150°).

KEY POINTS Key points of this section

- Potential V = work per unit charge brought from infinity; unit: the volt ($1 \text{ V} = 1 \text{ J C}^{-1}$).
- Work done in moving q through a p.d.: $W = qV$; watch the sign conventions (field vs

external agent).

- Uniform field: $E = V/d$, directed from high to low potential; equipotentials are perpendicular to field lines.
- Freely accelerated charge: $\frac{1}{2}mv^2 = qV$ — the energy method behind electron guns.
- Dipole: $p = q \times \text{separation}$, directed from $-$ to $+$; torque $\tau = pE \sin \theta$; stable equilibrium when aligned with $\vec{E}$.


With the language of potential and energy now in place, we are ready for the central object of this chapter: the capacitor, a device engineered precisely to separate charge and store energy in an electric field.

2 CAPACITORS, CAPACITANCE AND PERMITTIVITY

In the previous section we saw how electric potential allows us to quantify the work done when a charge moves in an electric field. We now turn to a device that stores electric charge and energy by maintaining a potential difference between two conductors: the capacitor. From the flash unit of a camera in a Yaoundé photography studio to the smoothing circuit inside your phone charger, capacitors are everywhere in modern electronics.

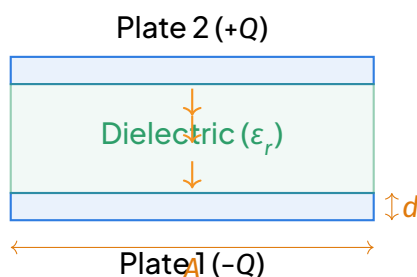2.1 What is a capacitor?

A **capacitor** consists of two conductors (called **plates**) separated by an insulating material known as a **dielectric**. When a voltage source is connected across the plates, one plate acquires a charge $+Q$ and the other $-Q$; the net charge of the capacitor as a whole remains zero. The dielectric prevents charge from flowing directly between the plates, so the charge is stored on the surfaces facing each other.



Parallel-plate capacitor: two conducting plates of area A separated by distance d , with a dielectric of relative permittivity ϵ_r . The electric field is uniform between the plates (fringing ignored).


Everyday examples abound:

- **Camera flash:** A capacitor charged to several hundred volts discharges rapidly through a xenon tube, producing an intense burst of light.

- **Radio tuning:** A variable capacitor in the LC circuit selects the desired frequency.
- **Phone charger / power supply:** Electrolytic capacitors smooth the rectified AC voltage, reducing ripple.
- **Power factor correction:** Large capacitors in industrial installations (e.g., at the ENEO sub-station in Douala) improve the power factor of inductive loads.

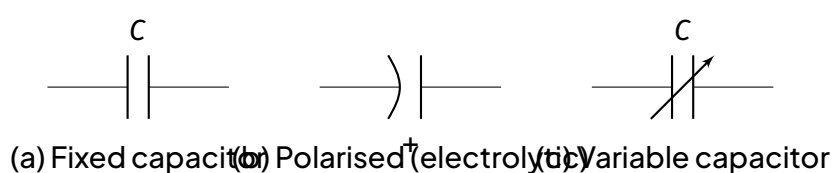2.2 Circuit symbols and identification

Capacitors are represented in circuit diagrams by specific symbols. It is essential to recognise them and to identify real components by their markings.



Standard circuit symbols for capacitors (European style). The polarised capacitor has a '+' mark on the positive terminal; the variable capacitor is shown with an arrow through the plates.

Identification of real components:

- **Fixed capacitors (ceramic, film, mica):** Usually marked with a three-digit code: the first two digits are the significant figures, the third is the multiplier (power of ten) in picofarads. Example: 104 means $10 \times 10^4 \text{ pF} = 100 \text{ nF} = 0.1 \mu\text{F}$. A letter may indicate tolerance (J = $\pm 5\%$, K = $\pm 10\%$, M = $\pm 20\%$).
- **Electrolytic capacitors:** Cylindrical with a clearly marked negative stripe (or positive '+' sign). The capacitance (in μF) and voltage rating (e.g., $470 \mu\text{F} 25\text{V}$) are printed on the body. Warning: Reversing the polarity can cause the capacitor to overheat and explode.
- **Variable capacitors:** Air-spaced or plastic-film types with a rotating shaft; used in tuning circuits. Capacitance varies typically from a few pF to a few hundred pF.

WARNING Polarity of electrolytic capacitors

Always observe the polarity markings when connecting an electrolytic capacitor in a DC circuit. Connecting it backwards can lead to catastrophic failure (venting, explosion). In AC or signal circuits, use non-polarised types (ceramic, film, or bipolar electrolytic).

2.3 Definition of capacitance and the farad

The ability of a capacitor to store charge per unit voltage is its **capacitance**.

DEFINITION Capacitance

The capacitance C of a capacitor is defined as the ratio of the magnitude of charge Q on one plate to the potential difference V between the plates:

$$C = \frac{Q}{V}$$

The SI unit of capacitance is the **farad** (symbol F): $1 \text{ F} = 1 \text{ C V}^{-1}$.

WARNING Charge Q in $C = Q/V$

Q is the charge on one plate only (the positive plate carries $+Q$, the negative plate $-Q$). It is not the sum of the charges on both plates (which would be zero). This is a frequent source of error in examinations.

The farad is a very large unit. Practical capacitors use submultiples:

$$1 \mu\text{F} = 10^{-6} \text{ F}, \quad 1 \text{ nF} = 10^{-9} \text{ F}, \quad 1 \text{ pF} = 10^{-12} \text{ F}.$$

KEY POINTS Unit conversion

Always convert μF , nF and pF to farads before substituting into formulas. For example, $4.7 \mu\text{F} = 4.7 \times 10^{-6} \text{ F}$. Forgetting this conversion is one of the most common mistakes in GCE Advanced Level papers.

2.4 The parallel-plate capacitor: factors affecting capacitance

The simplest capacitor to analyse is the parallel-plate capacitor: two large conducting plates of area A , separated by a small distance d (so that edge effects are negligible). Let the dielectric between the plates have relative permittivity ϵ_r .

PROPERTY Derivation of capacitance for a parallel-plate capacitor (examinable)

Using Gauss's law, consider a Gaussian pillbox that encloses part of the positive plate. The electric flux passes only through the face inside the capacitor (field is zero inside the conductor and negligible outside). If $\sigma = Q/A$ is the surface charge density:

$$\oint \vec{E} \cdot d\vec{A} = \frac{Q_{\text{enc}}}{\epsilon_0 \epsilon_r} \implies EA = \frac{\sigma A}{\epsilon_0 \epsilon_r}$$

Hence the uniform electric field between the plates is

$$E = \frac{\sigma}{\epsilon_0 \epsilon_r} = \frac{Q}{\epsilon_0 \epsilon_r A}.$$

The potential difference is $V = Ed$ (since the field is uniform). Therefore

$$V = \frac{Qd}{\epsilon_0 \epsilon_r A} \implies C = \frac{Q}{V} = \frac{\epsilon_0 \epsilon_r A}{d}.$$

DEFINITION Relative permittivity (dielectric constant)

The **relative permittivity** ϵ_r of a material is defined as the ratio of the capacitance of a capacitor with that material as dielectric to the capacitance of the same capacitor with vacuum (or air, to a very good approximation) as dielectric:

$$\epsilon_r = \frac{C_{\text{dielectric}}}{C_{\text{vacuum}}}.$$

For a parallel-plate capacitor,

$$C = \frac{\epsilon_0 \epsilon_r A}{d},$$

where $\epsilon_0 = 8.85 \times 10^{-12} \text{ F m}^{-1}$ is the permittivity of free space.

PROPERTY Factors affecting the capacitance of a parallel-plate capacitor

- Plate area A : $C \propto A$. Larger plates store more charge for a given voltage.
- Separation d : $C \propto 1/d$. Bringing plates closer increases the field for the same charge, reducing V and increasing C .
- Dielectric material (ϵ_r): $C \propto \epsilon_r$. Inserting a dielectric increases capacitance by a factor ϵ_r .

These relationships hold qualitatively for other geometries as well (cylindrical, spherical capacitors).

2.5 Action of a dielectric: polarisation

When a dielectric is placed in an electric field, its molecules become **polarised**: positive and negative charges within each molecule are slightly displaced, creating induced dipoles. In a polar dielectric (e.g., water), permanent dipoles align with the field; in a non-polar dielectric (e.g., polyethylene), dipoles are induced.

The net effect is a layer of induced charge on the dielectric surfaces adjacent to the plates. This induced charge produces an electric field opposing the original field, reducing the net field inside the dielectric by a factor ϵ_r . Since $V = Ed$, the potential difference for a given charge Q decreases, so $C = Q/V$ increases.

DID YOU KNOW? Dielectric strength

Every dielectric has a maximum electric field it can withstand without breaking down (becoming conductive). This is the **dielectric strength**, typically in V m^{-1} or kV mm^{-1} . For air it is about $3 \times 10^6 \text{ V m}^{-1}$; for mica $\sim 10^8 \text{ V m}^{-1}$. Exceeding this limit causes a spark or permanent damage. Capacitors are rated with a maximum working voltage.

Typical values of ϵ_r at room temperature:


Material	Relative permittivity ϵ_r
Vacuum	1 (by definition)
Air (STP)	$1.0006 \approx 1$
Paper (impregnated)	2–4
Mica	5–7
Glass	5–10
Ceramics (Class 1)	10–100
Ceramics (Class 2, high-K)	1000–5000
Water (pure, 20°C)	80

2.6 Measurement of capacitance

The most direct method uses the definition $C = Q/V$. We can measure Q and V simultaneously.

METHOD Measuring capacitance by constant-current charging

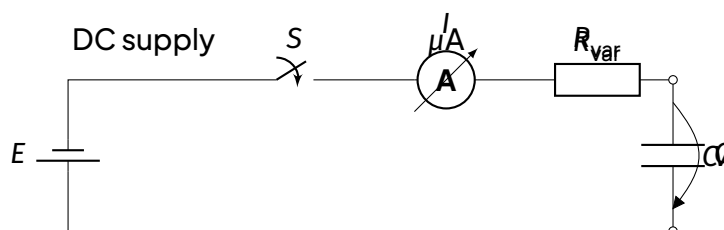
1. Set up the circuit: a DC supply, a switch, a microammeter (or coulombmeter) in series with the capacitor C , a variable resistor to maintain constant current, and a voltmeter across C .
2. Close the switch and adjust the variable resistor to give a constant charging current I (the current will naturally decrease as the capacitor charges; the resistor must be adjusted continuously, or a constant-current source used).
3. Start a stopwatch as the switch is closed. Record the time t when the voltmeter reads a chosen voltage V .
4. The charge delivered is $Q = It$ (since I is constant).
5. Calculate $C = Q/V = It/V$.
6. Repeat for several (V, t) pairs and plot Q vs V ; the gradient gives C .



Experimental circuit for measuring capacitance by constant-current charging. The variable resistor R_{var} is adjusted to keep the current I constant. The voltmeter measures the voltage V across the capacitor.

METHOD Alternative: Reed switch method (common in school laboratories)

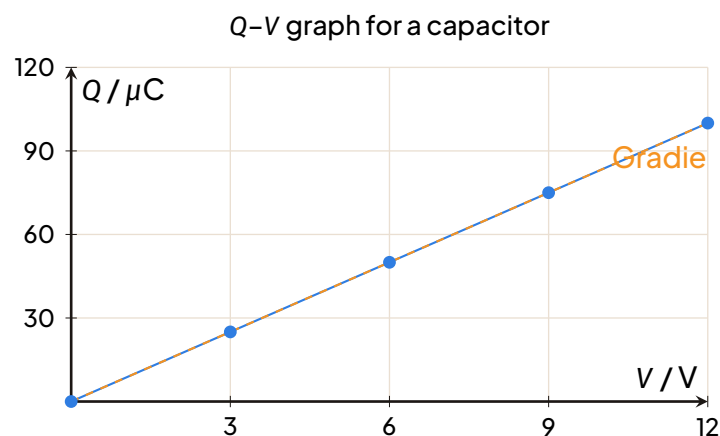1. A reed switch driven at a known frequency f alternately charges the capacitor from a battery of voltage V and discharges it through a microammeter.
2. The average current measured is $I = Qf = CVf$.
3. Hence $C = I/(Vf)$.



Q versus V graph for a capacitor. The graph is a straight line through the origin; its gradient equals the capacitance C .

2.7 Worked examples

WORKED EXAMPLE 3 Capacitance of a parallel-plate capacitor

A parallel-plate capacitor has plates of area $A = 200 \text{ cm}^2$ separated by a distance $d =$

0.50 mm. The space between the plates is filled with mica of relative permittivity $\epsilon_r = 6.0$. Calculate:

1. the capacitance C ,
2. the charge on each plate when the capacitor is connected to a 12 V battery,
3. the electric field strength between the plates.

SOLUTION

Solution:

1. Convert to SI units: $A = 200 \text{ cm}^2 = 200 \times 10^{-4} \text{ m}^2 = 0.0200 \text{ m}^2$, $d = 0.50 \text{ mm} = 0.50 \times 10^{-3} \text{ m} = 5.0 \times 10^{-4} \text{ m}$.

$$C = \frac{\epsilon_0 \epsilon_r A}{d} = \frac{(8.85 \times 10^{-12}) \times 6.0 \times 0.0200}{5.0 \times 10^{-4}} = \frac{1.062 \times 10^{-12}}{5.0 \times 10^{-4}} = 2.124 \times 10^{-9} \text{ F} = 2.12 \text{ nF}.$$

2. $Q = CV = (2.124 \times 10^{-9}) \times 12 = 2.55 \times 10^{-8} \text{ C} = 25.5 \text{ nC}$.
3. $E = V/d = 12/(5.0 \times 10^{-4}) = 2.4 \times 10^4 \text{ V m}^{-1}$. (Alternatively, $E = \sigma/(\epsilon_0 \epsilon_r) = Q/(\epsilon_0 \epsilon_r A)$ gives the same result.)

WORKED EXAMPLE 4 Effect of dielectric insertion on an isolated capacitor

A parallel-plate capacitor with air dielectric ($\epsilon_r = 1$) is charged to a potential difference V_0 and then disconnected from the supply. A dielectric slab of relative permittivity $\epsilon_r = 4$ is inserted completely between the plates. Determine the new:

1. capacitance,
2. potential difference,
3. electric field,
4. energy stored.

Express each in terms of the initial values C_0 , V_0 , E_0 , U_0 .

SOLUTION

Solution: Since the capacitor is isolated, the charge Q remains constant.

1. $C = \epsilon_r C_0 = 4C_0$.
2. $V = Q/C = Q/(\epsilon_r C_0) = V_0/\epsilon_r = V_0/4$.
3. $E = V/d = (V_0/4)/d = E_0/4$.
4. $U = \frac{1}{2}QV = \frac{1}{2}Q(V_0/4) = U_0/4$. Note: The energy decreases. The “missing” energy is the

work done by the electric field in pulling the dielectric into the capacitor (the dielectric is attracted between the plates).

2.8 Summary of key points

KEY POINTS Key points for Section 2

- A capacitor stores charge on two conductors separated by a dielectric. Circuit symbols distinguish fixed, polarised (electrolytic) and variable capacitors.
- Capacitance $C = Q/V$; unit: farad (F). Submultiples: μF , nF, pF.
- For a parallel-plate capacitor: $C = \epsilon_0 \epsilon_r A/d$. Capacitance increases with plate area A and ϵ_r , decreases with separation d .
- Relative permittivity $\epsilon_r = C_{\text{dielectric}}/C_{\text{vacuum}}$. Typical values: air ≈ 1 , paper 2–4, mica 5–7, ceramics up to thousands.
- A dielectric polarises in an electric field, reducing the net field and increasing capacitance.
- Capacitance can be measured by charging with a constant current I for time t ($Q = It$) and measuring V , then $C = It/V$. A Q - V graph is a straight line through the origin with gradient C .
- Exam traps: Q is charge on one plate only; always convert submultiples to farads; observe polarity of electrolytic capacitors; distinguish between isolated capacitor (constant Q) and capacitor connected to battery (constant V) when a dielectric is inserted.

EXERCISE 2 Practice questions

1. A $10\ \mu\text{F}$ capacitor is charged to $24\ \text{V}$. Calculate the charge stored on one plate and the energy stored. (Energy formula will be covered in the next section.)
2. A parallel-plate capacitor with air dielectric has capacitance C_0 . The plate separation is halved and the space is filled with a dielectric of $\epsilon_r = 4$. What is the new capacitance in terms of C_0 ?
3. In a constant-current charging experiment, a current of $50\ \mu\text{A}$ flows for $2.0\ \text{s}$ and the voltage across the capacitor reaches $5.0\ \text{V}$. Determine the capacitance.
4. Explain why the capacitance of a capacitor increases when a dielectric is inserted, in

terms of polarisation and the electric field.

5. A ceramic capacitor is marked 473K. State its capacitance and tolerance.
6. A parallel-plate capacitor is charged to 100 V and then disconnected. The plate separation is doubled. What is the new voltage? (Assume air dielectric.)
7. Describe how you would use a reed switch and a microammeter to measure the capacitance of a capacitor. State the formula used.

SOLUTION Exercise 2


1. $Q = CV = 10 \times 10^{-6} \times 24 = 2.4 \times 10^{-4} \text{ C} = 240 \mu\text{C}$.
2. $C = \epsilon_0 \epsilon_r A/d$. Halving d doubles C ; multiplying by $\epsilon_r = 4$ quadruples it. New $C = 8C_0$.
3. $Q = It = 50 \times 10^{-6} \times 2.0 = 1.0 \times 10^{-4} \text{ C}$. $C = Q/V = 1.0 \times 10^{-4} / 5.0 = 2.0 \times 10^{-5} \text{ F} = 20 \mu\text{F}$.
4. The dielectric polarises, creating induced surface charges that produce an opposing field. The net field $E = E_0/\epsilon_r$ decreases, so for the same charge Q , $V = Ed$ decreases, hence $C = Q/V$ increases by factor ϵ_r .
5. Code 473: $47 \times 10^3 \text{ pF} = 47 \text{ nF} = 0.047 \mu\text{F}$. Letter K means $\pm 10\%$ tolerance.
6. Isolated capacitor $\Rightarrow Q$ constant. $C \propto 1/d$, so doubling d halves C . $V = Q/C$, so V doubles: new voltage = 200 V.
7. The reed switch charges the capacitor from a battery of voltage V at frequency f , then discharges it through the microammeter. Average current $I = Qf = CVf$. Hence $C = I/(Vf)$. Measure I , V , and f to find C .

3 COMBINATIONS OF CAPACITORS AND ENERGY STORED

In the previous section, we established that a single capacitor is characterised by its capacitance C , defined as the ratio of the charge Q stored on one plate to the potential difference V across it: $C = Q/V$. We also saw how the geometry of the plates and the dielectric material (through the relative permittivity ϵ_r) determine this capacitance. In real circuits — whether in a power supply smoothing circuit in a Douala electronics workshop or the flash unit of a camera — capacitors are rarely used alone. They are combined in networks. Understanding how to replace a network by a single equivalent capacitor, and how energy is distributed and stored, is essential for both the GCE examination and practical design.

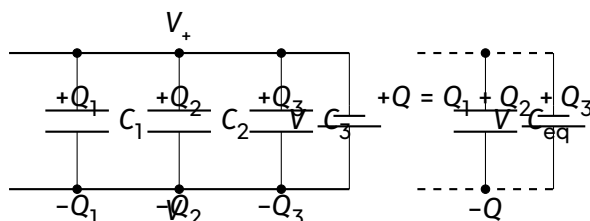3.1 Capacitors in parallel

Imagine connecting three capacitors side by side so that all their positive plates are joined to one conductor (at potential V_+) and all their negative plates to another conductor (at potential V_-). This is a **parallel combination**.



Capacitors in parallel: same potential difference V , charges add up.

Key observation: The potential difference across each capacitor is exactly the same and equal to the supply voltage V . However, the charge stored on each capacitor depends on its individual capacitance: $Q_1 = C_1 V$, $Q_2 = C_2 V$, $Q_3 = C_3 V$.

The total charge Q drawn from the supply is the sum of the charges on each capacitor:

$$Q = Q_1 + Q_2 + Q_3 = C_1 V + C_2 V + C_3 V = (C_1 + C_2 + C_3)V.$$

By definition, the equivalent capacitance C_{eq} of the combination is $C_{eq} = Q/V$. Therefore:

PROPERTY Equivalent Capacitance in Parallel

For capacitors connected in parallel, the potential difference across each is the same, and the equivalent capacitance is the sum of the individual capacitances:

$$C_{eq} = C_1 + C_2 + C_3 + \dots$$

The equivalent capacitance is always larger than the largest individual capacitance. This is physically intuitive: connecting plates in parallel effectively increases the total plate area A , and since $C \propto A$, the capacitance increases.

EXAMPLE Parallel Network Calculation

Three capacitors of capacitances $2\ \mu\text{F}$, $3\ \mu\text{F}$ and $5\ \mu\text{F}$ are connected in parallel across a $12\ \text{V}$ battery. Find:


1. The equivalent capacitance.
2. The charge on each capacitor.
3. The total charge drawn from the battery.

Solution:

1. $C_{\text{eq}} = 2 + 3 + 5 = 10 \mu\text{F}$.
2. Since $V = 12 \text{ V}$ across each: $Q_1 = C_1 V = 2 \times 12 = 24 \mu\text{C}$, $Q_2 = 3 \times 12 = 36 \mu\text{C}$, $Q_3 = 5 \times 12 = 60 \mu\text{C}$.
3. $Q_{\text{total}} = C_{\text{eq}} V = 10 \times 12 = 120 \mu\text{C}$. (Check: $24 + 36 + 60 = 120 \mu\text{C}$.)

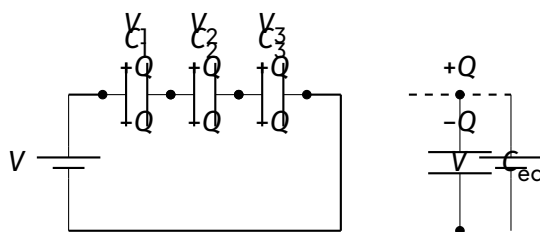3.2 Capacitors in series

Now connect the capacitors end-to-end: the negative plate of C_1 to the positive plate of C_2 , the negative of C_2 to the positive of C_3 , and so on. The outer plates connect to the battery terminals.



Capacitors in series: same charge Q on each, potential differences add up.

Key observation: When the battery is connected, electrons flow onto the first plate ($-Q$) and off the last plate ($+Q$). The isolated plates in between (the negative plate of C_1 and positive plate of C_2 , etc.) cannot exchange charge with the outside circuit. By conservation of charge and induction, the magnitude of charge Q on **every** capacitor in a series chain is identical.

The potential differences add up: $V = V_1 + V_2 + V_3$. Since $V_1 = Q/C_1$, $V_2 = Q/C_2$, $V_3 = Q/C_3$, we have:

$$V = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3} = Q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right).$$

The equivalent capacitance satisfies $V = Q/C_{\text{eq}}$, so:

PROPERTY Equivalent Capacitance in Series

For capacitors connected in series, the charge Q on each capacitor is the same, and the reciprocal of the equivalent capacitance is the sum of the reciprocals of the individual capacitances:

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

The equivalent capacitance is always smaller than the smallest individual capacitance. Physically, the effective plate separation d increases (the gaps add up), and since $C \propto 1/d$, the capacitance decreases.

EXAMPLE Series Network Calculation

Three capacitors of $2\ \mu\text{F}$, $3\ \mu\text{F}$ and $6\ \mu\text{F}$ are connected in series across a $12\ \text{V}$ battery. Find:

1. The equivalent capacitance.
2. The charge on each capacitor.
3. The potential difference across each capacitor.

Solution:

1. $\frac{1}{C_{\text{eq}}} = \frac{1}{2} + \frac{1}{3} + \frac{1}{6} = \frac{3+2+1}{6} = 1 \Rightarrow C_{\text{eq}} = 1\ \mu\text{F}.$
2. $Q = C_{\text{eq}}V = 1 \times 12 = 12\ \mu\text{C}.$ This same charge is on C_1 , C_2 and C_3 .
3. $V_1 = Q/C_1 = 12/2 = 6\ \text{V}, V_2 = 12/3 = 4\ \text{V}, V_3 = 12/6 = 2\ \text{V}.$ Check: $6 + 4 + 2 = 12\ \text{V}.$

3.3 Comparison with resistors: a classic trap**WARNING Resistors vs. Capacitors – Rules are Reversed!**

This is one of the most frequent sources of errors in the GCE examination. Memorise this table:

Combination	Resistors (R)	Capacitors (C)
Series	$R_{\text{eq}} = R_1 + R_2 + \dots$ (Increases)	$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$ (Decreases)
Parallel	$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$ (Decreases)	$C_{\text{eq}} = C_1 + C_2 + \dots$ (Increases)

Mnemonic: “Capacitors in parallel add like resistors in series (simple sum). Capacitors in series add like resistors in parallel (reciprocal sum).”


3.4 Mixed networks: a step-by-step reduction method

Real circuits often contain a mixture of series and parallel connections. The strategy is to simplify the network step by step, replacing identified sub-combinations by their equivalent capacitance, until a single C_{eq} remains.

METHOD Reducing a Capacitor Network (4 Steps)

1. Identify a sub-combination that is purely series or purely parallel (no other branches connected to the intermediate nodes).

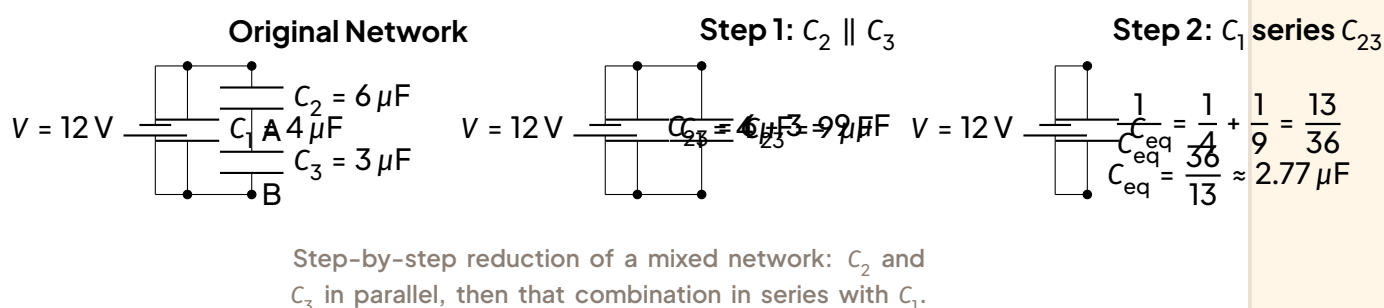2. Replace that sub-combination by its equivalent capacitance (C_{eq}). Redraw the circuit diagram – this is crucial for clarity.
3. Repeat steps 1 and 2 until only one equivalent capacitor remains across the supply terminals.
4. Work backwards (if individual charges/voltages are needed): Start from the total $Q_{total} = C_{eq} V_{supply}$ and distribute charge/voltage back through the steps using the rules: Series $\rightarrow$ same Q ; Parallel $\rightarrow$ same V .



WORKED EXAMPLE 5 Mixed Network Analysis

In the network shown above ($C_1 = 4 \mu\text{F}$, $C_2 = 6 \mu\text{F}$, $C_3 = 3 \mu\text{F}$, $V = 12 \text{ V}$), determine:

1. The total charge supplied by the battery.
2. The charge on and potential difference across each capacitor.

SOLUTION

Solution:

1. From the reduction: $C_{eq} = 36/13 \mu\text{F}$. $Q_{total} = C_{eq} V = \frac{36}{13} \times 12 = \frac{432}{13} \approx 33.2 \mu\text{C}$.
2. Work backwards:
 - Step 2 (Series C_1 and C_{23}): Same charge Q_{total} flows through both. $Q_1 = Q_{23} = 33.2 \mu\text{C}$. $V_1 = Q_1/C_1 = 33.2/4 = 8.31 \text{ V}$. $V_{23} = Q_{23}/C_{23} = 33.2/9 = 3.69 \text{ V}$. (Check: $8.31 + 3.69 \approx 12 \text{ V}$.)
 - Step 1 (Parallel C_2 and C_3): Same voltage $V_{23} = 3.69 \text{ V}$ across both. $Q_2 = C_2 V_{23} = 6 \times 3.69 = 22.1 \mu\text{C}$. $Q_3 = C_3 V_{23} = 3 \times 3.69 = 11.1 \mu\text{C}$. (Check: $Q_2 + Q_3 = 33.2 \mu\text{C} = Q_{23}$.)

3.5 Energy stored in a capacitor


When a capacitor is charged, work is done by the battery (or external agent) to move charge

against the growing potential difference. This work is stored as electrostatic potential energy in the electric field between the plates.

Consider the charging process. At an intermediate stage, the capacitor has charge q and potential difference $v = q/C$. To add a small charge dq , the work done is $dW = v dq = \frac{q}{C} dq$. The total work to charge from 0 to Q is:

$$W = \int_0^Q \frac{q}{C} dq = \frac{1}{C} \left[\frac{q^2}{2} \right]_0^Q = \frac{Q^2}{2C}.$$

This is exactly the area under the V - Q graph (a straight line through the origin).

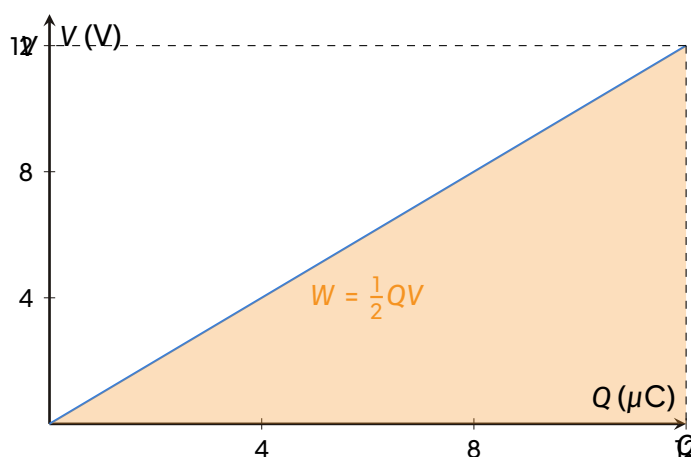

The V - Q graph for a capacitor. The shaded triangular area represents the energy stored $W = \frac{1}{2}QV$.

Using $Q = CV$, we obtain three equivalent forms for the stored energy:

KEY POINTS Energy Stored in a Capacitor

The electrostatic energy W stored in a charged capacitor can be expressed in three equivalent forms:

$$W = \frac{1}{2}QV = \frac{1}{2}CV^2 = \frac{Q^2}{2C}$$

Units: Joule (J).

Where is the energy? It resides in the electric field between the plates. For a parallel-plate capacitor, the energy density (energy per unit volume) is $u = \frac{1}{2}\epsilon_0\epsilon_r E^2$. This concept is fundamental in electromagnetism.

EXAMPLE Energy Calculations

A $10 \mu\text{F}$ capacitor is charged to 100 V .

1. Calculate the energy stored.

2. The capacitor is then disconnected from the supply and the plate separation is doubled (capacitance halves). What is the new energy? Explain the change.

Solution:

1. $W = \frac{1}{2}CV^2 = 0.5 \times 10 \times 10^{-6} \times 100^2 = 0.05 \text{ J} = 50 \text{ mJ}.$
2. Disconnected $\Rightarrow$ Charge Q is constant. $C' = C/2 = 5 \mu\text{F}$. $W' = \frac{Q^2}{2C'} = \frac{Q^2}{2(C/2)} = \frac{Q^2}{C} = 2 \times \frac{Q^2}{2C} = 2W = 0.10 \text{ J}.$ The energy doubles. The extra energy comes from the work done by the external agent pulling the plates apart against the attractive electrostatic force.

3.6 Energy in combinations and dissipation

Energy in series and parallel combinations. Since energy is a scalar, the total energy stored in a network is simply the sum of the energies stored in each capacitor: $W_{\text{total}} = \sum \frac{1}{2}C_i V_i^2 = \sum \frac{Q_i^2}{2C_i}$. This must equal the energy stored in the equivalent capacitor: $W_{\text{eq}} = \frac{1}{2}C_{\text{eq}} V_{\text{supply}}^2$. This provides a useful check for your calculations.

Energy dissipation during charging. A surprising and examinable result: when a capacitor is charged from a battery of constant voltage V through a resistor (or even ideal wires with radiation resistance), the battery supplies energy $W_{\text{batt}} = QV = CV^2$. The capacitor stores only $W_{\text{cap}} = \frac{1}{2}CV^2$. **Half the energy supplied by the battery is dissipated as heat in the connecting wires/resistor (or radiated).** This is independent of the resistance value!

WARNING The “Missing Half” Energy

Never assume the energy supplied by the battery equals the energy stored in the capacitor.

- Battery supplies: $W_{\text{supplied}} = QV = CV^2$.
- Capacitor stores: $W_{\text{stored}} = \frac{1}{2}CV^2$.
- Energy dissipated (heat/radiation): $W_{\text{dissipated}} = \frac{1}{2}CV^2$.

This is a favourite GCE multiple-choice and explanation question.

Connecting charged capacitors (qualitative). If a charged capacitor C_1 (charge Q_0 , voltage V_0) is connected in parallel to an uncharged capacitor C_2 , charge redistributes until the voltages equalise. The final voltage is $V_f = Q_0 / (C_1 + C_2)$. The final energy is $W_f = \frac{1}{2}(C_1 + C_2)V_f^2 = \frac{1}{2} \frac{Q_0^2}{C_1 + C_2}$. The initial energy was $W_i = \frac{1}{2} \frac{Q_0^2}{C_1}$. Since $C_1 + C_2 > C_1$, $W_f < W_i$. The “lost” energy is dissipated as heat in

the connecting wires (and spark if contact is made abruptly). **Charge is conserved; energy is not conserved in the capacitor system alone.**

WORKED EXAMPLE 6 Energy Redistribution

A $4\ \mu\text{F}$ capacitor is charged to $200\ \text{V}$. It is then disconnected from the supply and connected in parallel with an uncharged $2\ \mu\text{F}$ capacitor. Find:

1. The final potential difference across the combination.
2. The initial and final total energy stored.
3. The energy dissipated.

SOLUTION

Solution:

1. Initial charge: $Q_0 = C_1 V_0 = 4 \times 10^{-6} \times 200 = 800\ \mu\text{C}$. After connection (parallel): $V_f = \frac{Q_0}{C_1 + C_2} = \frac{800}{6} = 133.3\ \text{V}$.
2. $W_i = \frac{1}{2} C_1 V_0^2 = 0.5 \times 4 \times 10^{-6} \times 200^2 = 0.08\ \text{J}$. $W_f = \frac{1}{2} (C_1 + C_2) V_f^2 = 0.5 \times 6 \times 10^{-6} \times (133.3)^2 \approx 0.0533\ \text{J}$.
3. $W_{\text{dissipated}} = W_i - W_f = 0.08 - 0.0533 = 0.0267\ \text{J}$.

DID YOU KNOW? Supercapacitors in Yaoundé Traffic Lights?

Modern “supercapacitors” (or ultracapacitors) can have capacitances of thousands of Farads (e.g., $3000\ \text{F}$) in a small can. They bridge the gap between electrolytic capacitors and batteries. In Cameroon, they are increasingly used in solar-powered street lighting systems (like those along the Yaoundé–Nsimalen highway) to provide high-current bursts for LED lamps and to smooth the intermittent solar input, lasting far longer than batteries in the harsh tropical heat. Their energy density is still lower than Li-ion batteries, but their power density and cycle life are unmatched.

EXERCISE 3 Practice Problems

1. Three capacitors $C_1 = 2\ \mu\text{F}$, $C_2 = 4\ \mu\text{F}$, $C_3 = 6\ \mu\text{F}$ are connected: C_1 and C_2 in series, and this series combination in parallel with C_3 . A $12\ \text{V}$ battery is connected across the whole network. Find (a) the equivalent capacitance, (b) the charge on C_3 , (c) the voltage across C_1 .
2. A $10\ \mu\text{F}$ capacitor charged to $50\ \text{V}$ is disconnected and then connected in series with

an uncharged $20\ \mu\text{F}$ capacitor (the two free outer plates are not connected to each other). Find the final charge on each and the final voltage across each. Hint: Is there a closed circuit for charge to flow?

3. Prove that the total energy stored in two capacitors connected in parallel across a battery V is exactly $\frac{1}{2}C_{\text{eq}}V^2$. Show that the energy supplied by the battery is $C_{\text{eq}}V^2$ and deduce the heat dissipated.

SOLUTION Exercise 1


1. (a) $C_{12} = \frac{C_1 C_2}{C_1 + C_2} = \frac{8}{6} = \frac{4}{3}\ \mu\text{F}$. $C_{\text{eq}} = C_{12} + C_3 = \frac{4}{3} + 6 = \frac{22}{3} \approx 7.33\ \mu\text{F}$. (b) C_3 is directly across battery: $V_3 = 12\ \text{V}$. $Q_3 = C_3 V_3 = 6 \times 12 = 72\ \mu\text{C}$. (c) Voltage across series branch $V_{12} = 12\ \text{V}$. Charge on series branch $Q_{12} = C_{12} V_{12} = \frac{4}{3} \times 12 = 16\ \mu\text{C}$. This is the charge on C_1 and C_2 . $V_1 = Q_{12}/C_1 = 16/2 = 8\ \text{V}$.
2. Isolated series connection (open circuit): The two inner plates are joined and isolated from the outer plates. The outer plates are not connected to each other. There is no closed circuit for charge to flow. Therefore, no redistribution occurs. The charged capacitor retains its charge $Q_1 = 500\ \mu\text{C}$ and voltage $V_1 = 50\ \text{V}$. The uncharged capacitor remains with $Q_2 = 0$ and $V_2 = 0\ \text{V}$.
3. Parallel combination: $W_{\text{total}} = \frac{1}{2}C_1 V^2 + \frac{1}{2}C_2 V^2 = \frac{1}{2}(C_1 + C_2)V^2 = \frac{1}{2}C_{\text{eq}}V^2$. Battery supplies charge $Q_{\text{total}} = C_{\text{eq}}V$ at constant V : $W_{\text{batt}} = Q_{\text{total}}V = C_{\text{eq}}V^2$. Dissipated = $W_{\text{batt}} - W_{\text{stored}} = \frac{1}{2}C_{\text{eq}}V^2$.

4 CHARGING AND DISCHARGING THROUGH A RESISTOR: THE TIME CONSTANT

In the previous section we saw how capacitors combine and how they store energy when connected to a d.c. supply. We implicitly assumed the charging happened instantly. In reality, every circuit has resistance — the internal resistance of the battery, the resistance of connecting wires, or a deliberately added resistor. This resistance limits the current and makes the charging (and discharging) a gradual process governed by a single, crucial parameter: the **time constant**. Understanding this transient behaviour is essential not only for the GCE examination but for designing timing circuits, camera flashes, and life-saving defibrillators.

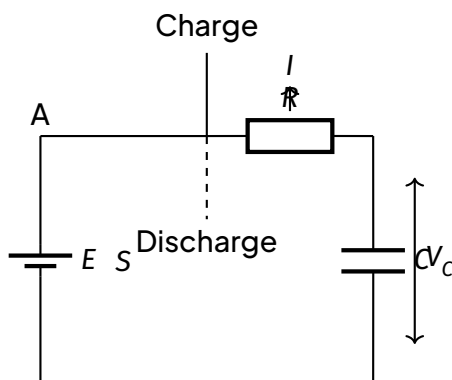4.1 The RC circuit: qualitative description

Consider a capacitor C connected in series with a resistor R and a d.c. source of e.m.f. E (negligible internal resistance). A two-way switch allows us to connect the capacitor either to the supply (position A: charging) or to a short circuit through the resistor (position B: discharging).



RC series circuit with a two-way switch. Position A (solid): charging from source E . Position B (dashed): discharging through R .

Charging (Switch at A): At the instant the switch closes ($t = 0$), the capacitor is uncharged ($V_C = 0$). The full e.m.f. E appears across the resistor, so the current is maximum: $I_0 = E/R$. As charge accumulates on the plates, V_C rises, opposing the supply. The voltage across the resistor ($V_R = E - V_C$) falls, so the current decreases. Eventually, $V_C \rightarrow E$, $V_R \rightarrow 0$, and $I \rightarrow 0$. The capacitor acts like an open circuit.

Discharging (Switch at B): With the capacitor fully charged to $Q_0 = CE$ ($V_C = E$), flipping the switch to B connects C directly across R . The capacitor drives a current through the resistor in the opposite direction to the charging current. V_C and I fall exponentially to zero. The capacitor acts like a temporary battery whose voltage decays.

4.2 The time constant $\tau = RC$

During these transients, the product RC appears naturally. It is called the **time constant** and denoted τ (tau).

DEFINITION Time constant τ

For a series RC circuit, the time constant is defined as

$$\tau = RC$$

where R is the resistance in ohms (Ω) and C is the capacitance in farads (F). The unit of τ is the **second** (s), since $\Omega \cdot F = \text{V A}^{-1} \cdot \text{C V}^{-1} = \text{C A}^{-1} = \text{s}$.

PROPERTY Physical meaning of τ

The time constant τ has three equivalent practical interpretations:

1. **Charging:** It is the time taken for the charge (or voltage) to rise to $(1 - e^{-1}) \approx 63.2\%$ of its final maximum value.

2. Discharging: It is the time taken for the charge (or voltage) to fall to $e^{-1} \approx 36.8\%$ of its initial value.
3. Initial slope (tangent method): It is the time the process would take to complete if the initial rate of change were maintained constant (the tangent at $t = 0$ intercepts the final value at $t = \tau$).

4.3 Mathematical equations for charging and discharging

We derive the equations using Kirchhoff's voltage law (KVL) and the definition of current $I = \frac{dQ}{dt}$.

1. Charging (Switch at A): KVL: $E = V_R + V_C = IR + \frac{Q}{C}$. Since $I = \frac{dQ}{dt}$, we have the differential equation:

$$E = R \frac{dQ}{dt} + \frac{Q}{C} \Rightarrow \frac{dQ}{dt} = \frac{E}{R} - \frac{Q}{RC} = \frac{1}{RC}(EC - Q).$$

Separating variables and integrating from $t = 0$ ($Q = 0$) to t (Q):

$$\int_0^Q \frac{dQ'}{EC - Q'} = \int_0^t \frac{dt'}{RC} \Rightarrow \left[-\ln(EC - Q') \right]_0^Q = \frac{t}{RC}.$$

$$-\ln(EC - Q) + \ln(EC) = \frac{t}{RC} \Rightarrow \ln\left(\frac{EC}{EC - Q}\right) = \frac{t}{RC}.$$

Solving for Q , and noting $Q_0 = CE$ (final charge) and $V_0 = E$ (final voltage):

$$Q = Q_0(1 - e^{-t/RC}), \quad V = V_0(1 - e^{-t/RC}).$$

Current $I = \frac{dQ}{dt} = \frac{Q_0}{RC} e^{-t/RC} = \frac{V_0}{R} e^{-t/RC} = I_0 e^{-t/RC}$ where $I_0 = V_0/R = E/R$.

2. Discharging (Switch at B): KVL: $0 = V_R + V_C = IR + \frac{Q}{C}$. Current flows out of the capacitor, so $I = -\frac{dQ}{dt}$ (if Q is charge on the positive plate).

$$0 = -R \frac{dQ}{dt} + \frac{Q}{C} \Rightarrow \frac{dQ}{dt} = -\frac{Q}{RC}.$$

Integrating from $t = 0$ ($Q = Q_0$) to t (Q):

$$\int_{Q_0}^Q \frac{dQ'}{Q'} = - \int_0^t \frac{dt'}{RC} \Rightarrow \ln \frac{Q}{Q_0} = -\frac{t}{RC}.$$

Hence:

$$Q = Q_0 e^{-t/RC}, \quad V = V_0 e^{-t/RC}.$$

Current magnitude $I = \left| \frac{dQ}{dt} \right| = \frac{Q_0}{RC} e^{-t/RC} = I_0 e^{-t/RC}$. The direction is opposite to the charging current.


PROPERTY The six exponential equations

Let $\tau = RC$, $Q_0 = CV_0$ (maximum charge), $I_0 = V_0/R$ (maximum current magnitude).


Quantity	Charging (from 0)	Discharging (from Q_0, V_0)
Charge Q	$Q = Q_0(1 - e^{-t/\tau})$	$Q = Q_0 e^{-t/\tau}$
Voltage V	$V = V_0(1 - e^{-t/\tau})$	$V = V_0 e^{-t/\tau}$
Current I	$I = I_0 e^{-t/\tau}$	$I = -I_0 e^{-t/\tau}$ (opposite direction)

PROPERTY Behaviour at limits

- At $t = 0$ (charging): $Q = 0, V = 0, I = I_0$ (maximum). The uncharged capacitor behaves like a short circuit (wire).
- As $t \rightarrow \infty$ (charging): $Q \rightarrow Q_0, V \rightarrow V_0, I \rightarrow 0$. The fully charged capacitor behaves like an open circuit (infinite resistance).
- At $t = 0$ (discharging): $Q = Q_0, V = V_0, I = -I_0$ (maximum, opposite direction to charging).
- As $t \rightarrow \infty$ (discharging): $Q \rightarrow 0, V \rightarrow 0, I \rightarrow 0$.

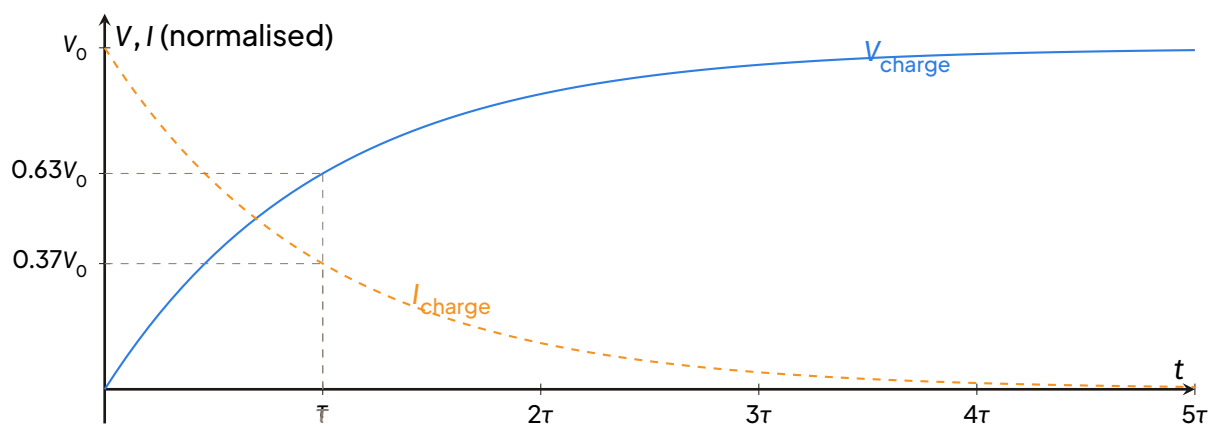

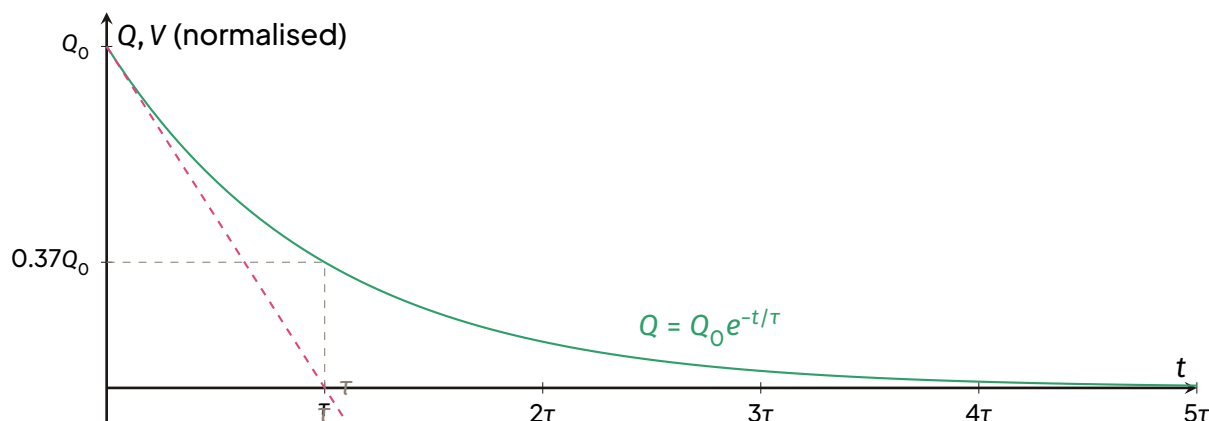Charging curves: Voltage $V(t)$ rises to 63% of V_0 at $t = \tau$; Current $I(t)$ falls to 37% of I_0 at $t = \tau$.



Discharging curve $Q(t)$. The tangent at $t = 0$ (gradient $-Q_0/\tau$) intercepts the time axis at $t = \tau$. At $t = \tau$, $Q = 0.37Q_0$.

4.4 Graphical analysis and determination of τ

In the laboratory (Paper 3 Practical), you will often determine τ from experimental data. Two graphical methods are standard.

METHOD Finding τ from a V - t or Q - t graph (Direct reading)

1. Plot the experimental points (V vs t for charging or discharging) and draw a smooth curve.
2. Charging: Find the final voltage V_0 (plateau). Calculate $0.63V_0$. Read the time t corresponding to this voltage on the curve. This t is τ .
3. Discharging: Find the initial voltage V_0 . Calculate $0.37V_0$. Read the time t corresponding to this voltage. This t is τ .
4. Tangent method (works for both): Draw the tangent to the curve at $t = 0$. Find where this tangent intersects the horizontal asymptote (V_0 for charging, 0 for discharging). The time coordinate of this intersection is τ .

METHOD Finding τ from a $\ln V$ vs t graph (Linearisation) — Core Practical Skill

For discharging: $V = V_0 e^{-t/RC}$. Taking natural logarithms:

$$\ln V = \ln V_0 - \frac{1}{RC}t.$$


This is a straight line equation $y = c + mx$ with:

- $y = \ln V$ (vertical axis)

- $x = t$ (horizontal axis)
- Gradient $m = -\frac{1}{RC} = -\frac{1}{\tau}$
- Intercept $c = \ln V_0$

Procedure:

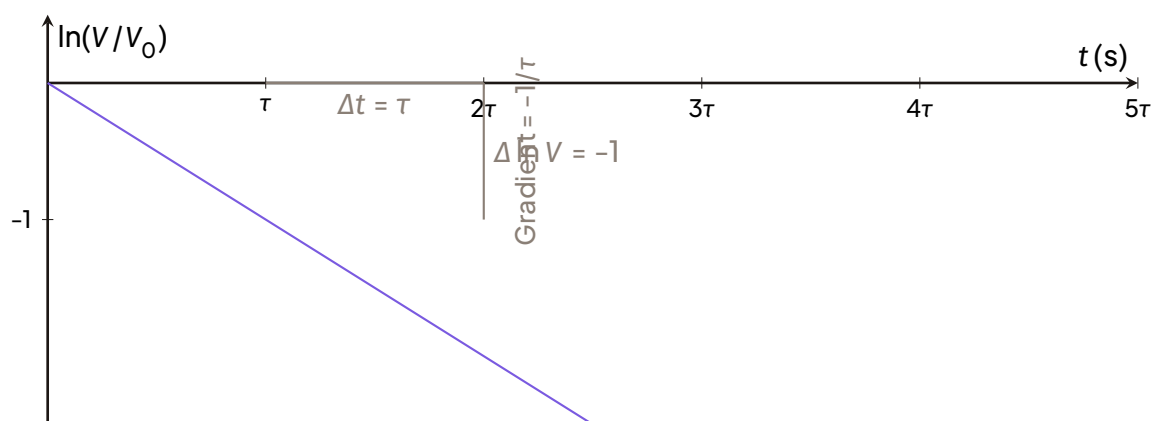1. Record V and t during discharge.
2. Calculate $\ln V$ for each reading.
3. Plot $\ln V$ (y-axis) against t (x-axis).
4. Draw the best-fit straight line.
5. Determine the gradient m (negative).
6. Calculate $\tau = -\frac{1}{m}$ and $C = \frac{\tau}{R}$ (if R is known).



Linearised discharge graph: $\ln V$ vs t . The gradient is $-1/\tau$. A gradient triangle of $\Delta t = \tau$ gives $\Delta \ln V = -1$.

4.5 Worked examples

WORKED EXAMPLE 7 Charging a capacitor

A $10 \mu\text{F}$ capacitor is charged through a $100 \text{ k}\Omega$ resistor from a 12 V d.c. supply.

1. Calculate the time constant τ .
2. Find the charge, voltage, and current at $t = \tau$.
3. How long does it take for the voltage to reach 9.0 V ?

SOLUTION

Solution:

1. $\tau = RC = (100 \times 10^3 \Omega) \times (10 \times 10^{-6} \text{ F}) = 1.0 \text{ s}.$
2. $Q_0 = CV_0 = 10 \times 10^{-6} \text{ F} \times 12 \text{ V} = 120 \times 10^{-6} \text{ C}.$ $I_0 = V_0/R = 12 \text{ V}/100 \times 10^3 \Omega = 120 \times 10^{-6} \text{ A}.$ At $t = \tau$:
 $Q = Q_0(1 - e^{-1}) = 120 \times 0.632 = 75.8 \times 10^{-6} \text{ C}.$ $V = V_0(1 - e^{-1}) = 12 \times 0.632 = 7.58 \text{ V}.$ $I = I_0 e^{-1} = 120 \times 0.368 = 44.2 \times 10^{-6} \text{ A}.$
3. Use $V = V_0(1 - e^{-t/\tau})$. $9.0 = 12(1 - e^{-t/1.0}) \Rightarrow 1 - e^{-t} = 0.75 \Rightarrow e^{-t} = 0.25$. $-t = \ln(0.25) = -\ln 4 \Rightarrow t = \ln 4 \approx 1.39 \text{ s}.$

WORKED EXAMPLE 8 Analysing discharge dataA capacitor discharges through a $22 \text{ k}\Omega$ resistor. The following data is recorded:

$t \text{ (s)}$	0	10	20	30	40
$V \text{ (V)}$	10.0	6.1	3.7	2.2	1.4

Determine the capacitance C using a graphical method.**SOLUTION**Solution: We linearise: $\ln V = \ln V_0 - t/RC$. Calculate $\ln V$:

$t \text{ (s)}$	0	10	20	30	40
$\ln V$	2.30	1.81	1.31	0.79	0.34

Plotting $\ln V$ vs t gives a straight line. Using the first and last points for gradient: $m = \frac{0.34 - 2.30}{40 - 0} = \frac{-1.96}{40} = -0.049 \text{ s}^{-1}$. $\tau = -\frac{1}{m} = \frac{1}{0.049} \approx 20.4 \text{ s}.$ $C = \frac{\tau}{R} = \frac{20.4}{22 \times 10^3} = 9.27 \times 10^{-4} \text{ F} = 927 \text{ }\mu\text{F}.$ (Using all points for a best-fit line would give a more accurate result, typically $\approx 930 \text{ }\mu\text{F}$).

4.6 Applications of RC circuits**DID YOU KNOW?** RC circuits in everyday life

- Camera flash units: A battery charges a capacitor slowly through a high resistance (high τ). Triggering the flash discharges the capacitor through the xenon tube with very low resistance (tiny $\tau \approx \text{ms}$), delivering a huge power pulse.
- Defibrillators: A capacitor charged to several kV discharges through the patient's chest

in a controlled time ($\tau \approx 5 - 10 \text{ ms}$) to reset the heart rhythm. The energy stored ($\frac{1}{2}CV^2$) is typically 200 – 360 J.

- **Smoothing / Filter circuits:** In power supplies, a large capacitor after a rectifier charges quickly (low R) and discharges slowly through the load (high R_{load}), reducing ripple voltage. The condition $RC \gg T$ (period of AC) is essential.
- **Car indicator flashers:** An RC timer circuit controls a relay. The capacitor charges until a threshold voltage triggers the relay to switch the lights and discharge the capacitor. The flash rate is set by τ .

4.7 Common mistakes and examination tips

WARNING Current direction in discharge

During discharge, the current flows from the positive plate of the capacitor, through the resistor, to the negative plate. This is opposite to the charging current direction. In equations, if charging current is defined as positive, discharge current is $I = -I_0 e^{-t/RC}$. Always state the direction clearly in exams.

WARNING Confusing the equations

- Charging: V and Q rise ($1 - e^{-t/\tau}$); I falls ($e^{-t/\tau}$).
- Discharging: V , Q , and I all fall ($e^{-t/\tau}$).
- Do not write $V = V_0 e^{-t/\tau}$ for charging voltage!

WARNING The "5 τ " rule

For all practical purposes, a capacitor is considered fully charged or fully discharged after 5τ (reaches $> 99\%$ or $< 1\%$). In multiple-choice questions, "fully charged" implies $t \gg \tau$ or $t = 5\tau$.

WARNING Logarithm base

The linearisation $\ln V = \ln V_0 - t/RC$ uses natural logarithms (base e). Using $\log_{10}$ gives a gradient of $-1/(2.303RC)$. Check the question: if it asks for a graph of $\log V$ vs t , clarify the

base or use $\ln$ (standard in physics).

4.8 Consolidation exercises

EXERCISE 4 Exercise 1: Charging transients

A $4.7 \mu\text{F}$ capacitor is connected in series with a $1.0 \text{ M}\Omega$ resistor and a 6.0 V battery.

1. Calculate the time constant.
2. Determine the maximum charge and maximum current.
3. Find the voltage across the capacitor and the current in the circuit 5.0 s after closing the switch.
4. Sketch graphs of $V_C(t)$ and $I(t)$ for $0 \leq t \leq 20 \text{ s}$, marking τ and the 63% point.

EXERCISE 5 Exercise 2: Discharge analysis

A charged capacitor is discharged through a $47 \text{ k}\Omega$ resistor. The voltage falls from 12.0 V to 4.4 V in 30 s .

1. Calculate the time constant τ .
2. Determine the capacitance C .
3. What percentage of the initial energy remains after 30 s ?

EXERCISE 6 Exercise 3: Practical linearisation

In an experiment to determine the capacitance of an unknown capacitor, a student discharges it through a $100 \text{ k}\Omega$ resistor and records the voltage V at time t .

$t(\text{s})$	0	5	10	15	20	25
$V(\text{V})$	10.0	6.1	3.7	2.2	1.4	0.8

1. Complete a table of $\ln V$ values.
2. Plot $\ln V$ against t (on graph paper) and draw the best-fit line.
3. Determine the gradient and hence the capacitance C .
4. Explain why the $\ln V$ vs t graph is preferred over the V vs t graph for determining C accurately.

4.9 Answers to consolidation exercises

SOLUTION Exercise 1

1. $\tau = RC = 1.0 \times 10^6 \times 4.7 \times 10^{-6} = 4.7 \text{ s}.$
2. $Q_0 = CV_0 = 4.7 \times 10^{-6} \times 6.0 = 28.2 \text{ nC}.$ $I_0 = V_0/R = 6.0/1.0 \times 10^6 = 6.0 \text{ nA}.$
3. $t = 5.0 \text{ s} \approx 1.06\tau.$ $V = 6.0(1 - e^{-5.0/4.7}) = 6.0(1 - e^{-1.064}) = 6.0(1 - 0.345) = 3.93 \text{ V}.$ $I = 6.0 \times 10^{-6} \times e^{-1.064} = 2.07 \text{ nA}.$
4. Graphs: V rises from 0 to 6V asymptotically, passing through 3.78 V at $t = 4.7 \text{ s}.$ I falls from 6.0 nA to 0, passing through 2.21 nA at $t = 4.7 \text{ s}.$

SOLUTION Exercise 2

1. $V = V_0 e^{-t/\tau} \Rightarrow 4.4 = 12.0 e^{-30/\tau}.$ $e^{-30/\tau} = 4.4/12.0 = 0.3667.$ $-30/\tau = \ln(0.3667) \approx -1.003.$ $\tau = 30/1.003 \approx 29.9 \text{ s}.$
2. $C = \tau/R = 29.9/47000 = 636 \text{ nF}.$
3. Energy $U \propto V^2.$ $U/U_0 = (V/V_0)^2 = (0.3667)^2 = 0.134 = 13.4 \text{ \%}.$

SOLUTION Exercise 3

1. $\ln V: 2.30, 1.81, 1.31, 0.79, 0.34, -0.22.$
2. Graph: Straight line with negative slope.
3. Gradient $m \approx \frac{-0.22 - 2.30}{25 - 0} = \frac{-2.52}{25} = -0.1008 \text{ s}^{-1}.$ $\tau = -1/m = 9.92 \text{ s}.$ $C = \tau/R = 9.92/100000 = 99.2 \text{ nF}.$
4. The $V-t$ graph is a steep curve; reading the time for a specific voltage (e.g., 3.7 V) has large uncertainty. The $\ln V-t$ graph is a straight line; the gradient uses all data points, averaging out random errors, giving a much more precise determination of τ and hence $C.$

KEY POINTS Key points for revision

- RC circuit: Resistor limits current, causing exponential charge/discharge.

- Time constant $\tau = RC$ (seconds). Physical meaning: 63% rise (charge) or 37% fall (discharge); tangent intercept time.
- Charging: $Q = Q_0(1 - e^{-t/\tau})$, $V = V_0(1 - e^{-t/\tau})$, $I = I_0 e^{-t/\tau}$. At $t = 0$: short circuit. $t \rightarrow \infty$: open circuit.
- Discharging: $Q = Q_0 e^{-t/\tau}$, $V = V_0 e^{-t/\tau}$, $I = -I_0 e^{-t/\tau}$ (reverse direction).
- Graphical methods: 63%/37% rule, tangent at $t = 0$, $\ln V$ vs t straight line (gradient = $-1/\tau$).
- Applications: Flash units (high energy, short τ), smoothing (long τ), timers, defibrillators.

5 INTEGRATION ACTIVITY

5.1 Aims of the activity

This integration activity brings together everything you have learned in this chapter in a single, realistic engineering task. By the end of it, you should be able to:

- combine capacitors in series and in parallel and compute the **equivalent capacitance** of a network;
- calculate the **charge** $Q = CV$ and the **energy** $W = \frac{1}{2}CV^2$ stored in a capacitor bank connected to a d.c. supply;
- use the **discharge equation** $V = V_0 e^{-t/RC}$ and the **time constant** $\tau = RC$ to predict how long a capacitor can power a load;
- choose components from a limited “catalogue” to meet a design specification, and justify every choice with a calculation;
- interpret the limits $t = 0$ and $t \rightarrow \infty$ of the discharge curve and sketch the full $V(t)$ graph;
- communicate a technical design clearly, including its assumptions and limitations, as expected in the problem-solving questions of the GCE Advanced Level paper.

5.2 Situation

EXAMPLE The emergency lamp of the Ngoa-Ekelle household

During the rainy season in Yaoundé, power cuts are frequent in the evening, exactly when students are revising. A young technician, Laetitia, wants to build a small emergency lamp delay circuit for her family’s house in Ngoa-Ekelle. The idea is simple: while the mains adaptor is working, a bank of capacitors is charged by a 12 V d.c. supply; the instant the power fails, a relay disconnects the supply and the capacitor bank discharges through a small white LED lamp, keeping it lit for a short time so that nobody is left in complete darkness.

Design specification. The LED lamp must remain usefully lit for at least 30 s after the power cut. The white LED used behaves as follows (idealised model):

- it conducts and lights as soon as the voltage across it reaches $V_{\text{on}} = 3.0 \text{ V}$;
- it stops emitting useful light when the voltage across the capacitor bank falls to the cut-off voltage $V_c = 3.0 \text{ V}$;
- while lit, it draws a current that we model as flowing through an equivalent series resistor R (the resistor Laetitia must choose), so the discharge obeys the usual law

$$V(t) = V_0 e^{-t/(RC)}, \quad V_0 = 12 \text{ V};$$

- the LED needs an average power of about $P_{\text{LED}} \approx 30 \text{ mW}$ during the 30 s to give useful

light.

Laetitia's catalogue (the only components available in her drawer):

Component	Available values	Remarks
Electrolytic capacitors	100 μF , 220 μF , 470 μF , 1000 μF	all rated 16 V maximum; several of each value available
Resistors	1 k Ω , 2.2 k Ω , 4.7 k Ω , 10 k Ω , 22 k Ω , 47 k Ω , 100 k Ω , 220 k Ω , 470 k Ω , 1 M Ω	$\pm 5\%$ tolerance
Supply	12 V d.c. adaptor	charges the bank before the cut

Safety constraint. No capacitor may ever be subjected to a voltage greater than its 16 V rating.

Working in groups, you must produce Laetitia's design: the capacitor arrangement, the resistor, all supporting calculations, a sketch of $V(t)$, and a 5-minute pitch presenting your solution and its limitations.

5.3 Tasks

- Choosing the arrangement.** A single 1000 μF capacitor is not enough to store the required energy. Propose a parallel combination of at least two catalogue capacitors giving an equivalent capacitance C between 2000 μF and 2500 μF . Compute C . Explain, in two sentences, why a parallel (and not series) arrangement is appropriate here, referring to the voltage rating and to the way capacitances combine.
- Charge and energy stored.** The bank is fully charged by the 12 V supply. Calculate the charge Q_0 stored and the energy W_0 available in the bank.
- Is the energy sufficient?** Estimate the energy the LED needs to shine for 30 s at 30 mW. Compare with W_0 and conclude. Why should the usable energy actually be taken as $\frac{1}{2}C(V_0^2 - V_c^2)$ rather than W_0 ? Recompute the comparison with this corrected value.
- Choosing the resistor.** The lamp must still be lit at $t = 30$ s, i.e. $V(30 \text{ s}) \geq V_c = 3.0 \text{ V}$. Using $V(t) = V_0 e^{-t/(RC)}$, show that the time constant must satisfy $\tau = RC \geq \frac{t}{\ln(V_0/V_c)}$, and compute the minimum value of τ . Deduce the minimum acceptable value of R , then choose the smallest catalogue resistor that satisfies the condition. Justify why this choice is a good compromise (a larger R would give longer light but too little current for the LED to be usefully bright).
- Verification.** With your chosen R and C , compute τ , the voltage $V(30 \text{ s})$, and the time t_c at which the voltage actually reaches 3.0 V. Confirm the specification is met.
- Interpreting the limits.** State the values of $V(t)$ and of the discharge current $I(t) = \frac{V_0}{R} e^{-t/(RC)}$

at $t = 0$ and as $t \rightarrow \infty$. Compute the initial current I_0 and check it is reasonable for a small LED circuit.

7. **Sketching the curve.** Sketch $V(t)$ for $0 \leq t \leq 3\tau$, marking V_0 , V_c , τ and t_c . Recall the graphical meaning of τ (tangent at the origin, value $0.37 V_0$ at $t = \tau$).
8. **Critical discussion.** Give two reasons why the real lamp might shine for a slightly shorter time than your prediction (think of the idealisations in the model). Suggest one improvement to the design.

5.4 Model answer

1. Choosing the arrangement.

We connect one $1000 \mu\text{F}$, one $470 \mu\text{F}$ and one $1000 \mu\text{F}$ capacitor in parallel. In parallel, the capacitances add:

$$C = C_1 + C_2 + C_3 = 1000 + 470 + 1000 = 2470 \mu\text{F} = 2.47 \times 10^{-3} \text{ F}.$$

This lies in the target band $2000\text{--}2500 \mu\text{F}$. A parallel arrangement is appropriate because every capacitor then sits directly across the same 12 V supply, which is safely below the 16 V rating, while the capacitances add to give a larger total; in series the equivalent capacitance would be smaller than the smallest capacitor, which is the opposite of what we need for energy storage at a fixed voltage.

2. Charge and energy stored.

$$Q_0 = CV_0 = 2.47 \times 10^{-3} \times 12 = 2.96 \times 10^{-2} \text{ C} \approx 30 \text{ mC}.$$

$$W_0 = \frac{1}{2} CV_0^2 = \frac{1}{2} \times 2.47 \times 10^{-3} \times 12^2 = 0.178 \text{ J} \approx 0.18 \text{ J}.$$

3. Is the energy sufficient?

Energy needed by the LED:

$$W_{\text{LED}} = P_{\text{LED}} t = 30 \times 10^{-3} \times 30 = 0.90 \text{ J}.$$

This is larger than $W_0 = 0.18 \text{ J}$: with the catalogue capacitors, the bank cannot supply 30 mW continuously for 30 s . The honest conclusion is that the LED must draw less average power (a high-efficiency LED at reduced brightness, or intermittent flashing), or the specification on brightness must be relaxed. Moreover, the usable energy is only the part released between 12 V and the cut-off 3.0 V :

$$W_{\text{usable}} = \frac{1}{2} C (V_0^2 - V_c^2) = \frac{1}{2} \times 2.47 \times 10^{-3} \times (144 - 9) = 0.167 \text{ J}.$$

This corresponds to an average available power over 30 s of $0.167/30 \approx 5.6 \text{ mW}$: enough for a small high-brightness LED glowing dimly, which is acceptable for an emergency “find-your-candle” lamp. Laetitia therefore keeps the design but states clearly in her pitch that the lamp gives reduced brightness, not full illumination.

WARNING A trap worth noticing

Comparing W_0 with $P_{\text{LED}} t$ and concluding “it works” without checking the numbers is the classic error. Always do the numerical comparison, and always subtract the energy left in the capacitor at the cut-off voltage: the charge remaining below V_c is useless to the load.

4. Choosing the resistor.

We require $V(t) \geq V_c$ at $t = 30$ s:

$$V_0 e^{-t/(RC)} \geq V_c \implies e^{-t/(RC)} \geq \frac{V_c}{V_0} \implies \frac{t}{RC} \leq \ln \frac{V_0}{V_c} \implies \tau = RC \geq \frac{t}{\ln(V_0/V_c)}.$$

Numerically, $\ln(12/3.0) = \ln 4 = 1.386$, so

$$\tau_{\min} = \frac{30}{1.386} = 21.6 \text{ s.}$$

Hence the resistance must satisfy

$$R \geq \frac{\tau_{\min}}{C} = \frac{21.6}{2.47 \times 10^{-3}} = 8.74 \text{ k}\Omega.$$

The catalogue resistors are 1 k Ω , 2.2 k Ω , 4.7 k Ω , 10 k Ω , 22 k Ω , ... The smallest value that meets $R \geq 8.74$ k Ω is $R = 10$ k Ω . A larger R would indeed discharge the bank more slowly (longer light), but the initial LED current $I_0 = V_0/R$ would become too small to produce useful light; 10 k Ω gives a safe and adequate initial current of 1.2 mA (see Task 6), making it the best compromise.

5. Verification.

$$\tau = RC = 10^4 \times 2.47 \times 10^{-3} = 24.7 \text{ s.}$$

$$V(30 \text{ s}) = 12 e^{-30/24.7} = 12 e^{-1.215} = 12 \times 0.297 = 3.6 \text{ V} \geq 3.0 \text{ V.} \checkmark$$

The actual cut-off time:

$$t_c = \tau \ln \frac{V_0}{V_c} = 24.7 \times 1.386 = 34.2 \text{ s} \geq 30 \text{ s.} \checkmark$$

The specification is met, with a safety margin of about 4 s.


6. Interpreting the limits.

At $t = 0$: $V = V_0 = 12$ V (the capacitor behaves like a full reservoir) and the current is maximal:

$$I_0 = \frac{V_0}{R} = \frac{12}{10^4} = 1.2 \text{ mA,}$$

a safe current for a small LED. As $t \rightarrow \infty$: $V \rightarrow 0$ and $I \rightarrow 0$ exponentially; the capacitor is fully discharged and the lamp is dark. The light fades gradually rather than switching off abruptly — a gentle warning that the energy is running out.

7. Sketching the curve.

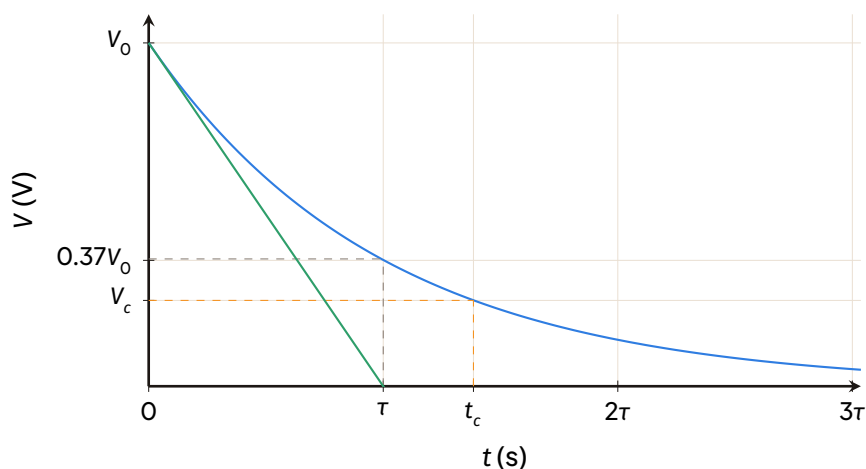

Discharge of the bank through $R = 10 \text{ k}\Omega$: $V(t) = 12e^{-t/24.7}$. The tangent at the origin (green) meets the time axis at $t = \tau$; the voltage crosses $V_c = 3.0 \text{ V}$ at $t_c \approx 34 \text{ s}$.

8. Critical discussion.

Possible reasons the real lamp shines for less than 34 s:

- **Component tolerances and leakage:** electrolytic capacitors have tolerances of typically $\pm 20\%$ and a small leakage current, so the real stored charge is less than computed; the resistors are only $\pm 5\%$.
- **Non-ideal LED model:** the LED does not draw current exactly like a fixed resistor; near the cut-off its current falls faster, and internal losses in the relay and wiring dissipate extra energy.

Improvement: add a fourth capacitor in parallel (e.g. another $1000 \mu\text{F}$, giving $C = 3470 \mu\text{F}$ and $t_c \approx 48 \text{ s}$), or use a flashing-LED circuit which draws power only in short pulses and can stretch the useful light well beyond a minute.

KEY POINTS

What this activity consolidates

- Parallel capacitances add: $C = C_1 + C_2 + \dots$; all share the supply voltage, which must stay below each rating.
- Stored quantities at voltage V_0 : $Q_0 = CV_0$, $W_0 = \frac{1}{2}CV_0^2$; usable energy down to cut-off: $\frac{1}{2}C(V_0^2 - V_c^2)$.
- Discharge law $V = V_0 e^{-t/RC}$ with $\tau = RC$; reaching a fraction V_c/V_0 takes $t_c = \tau \ln(V_0/V_c)$.
- A real design ends with a numerical verification and an honest discussion of the model's limits.

6 METHODS AND WORKED EXAMPLES

7 CAPACITORS

7.1 Skill 1 — Work done and potential energy of a charge in a uniform field

DEFINITION Electric Potential and Potential Difference

The **electric potential** V at a point is the work done per unit positive charge in bringing a small test charge from infinity to that point. The **potential difference** (p.d.) $V_{AB} = V_A - V_B$ between two points A and B is the work done per unit charge in moving a charge from B to A:

$$V_{AB} = \frac{W_{B \rightarrow A}}{q}.$$

Unit: the volt ($V = \text{J C}^{-1}$). In a uniform field $\vec{E}$, $V_{AB} = E d \cos \theta$ where d is the displacement from B to A and θ the angle between $\vec{E}$ and the displacement.

PROPERTY Work and Energy in a Uniform Field

For a charge q displaced from A to B in a uniform electric field $\vec{E}$:

- Work done by the electric force: $W_{AB} = q E d \cos \theta = q(V_A - V_B) = -q V_{BA}$.
- Change in electric potential energy: $\Delta E_p = E_{p,B} - E_{p,A} = -W_{AB} = q(V_B - V_A)$.
- Work done by an external agent moving the charge slowly (no change in kinetic energy): $W_{\text{ext}} = \Delta E_p = q(V_B - V_A)$.

Examinable derivation: $W = \int \vec{F} \cdot d\vec{l} = q \int \vec{E} \cdot d\vec{l} = q(V_A - V_B)$.

METHOD Work and potential in a uniform electric field

1. Draw the field. Sketch the plates or the region, mark the direction of $\vec{E}$ (from + plate to - plate) and the displacement $\vec{d}$ of the charge.
2. Compute the field if needed: $E = \frac{V}{d}$ between parallel plates separated by d at p.d. V .
3. Force on the charge: $\vec{F} = q\vec{E}$, magnitude $F = |q|E$. Direction: same as $\vec{E}$ if $q > 0$, opposite if $q < 0$.

4. Work of the electric force for a displacement from A to B:

$$W_{AB} = q E d \cos \theta = q(V_A - V_B) = -q V_{BA}$$

where θ is the angle between $\vec{F}$ (or $\vec{E}$ for $q > 0$) and the displacement. If the charge moves along the force, the field does positive work; if it moves against the force, the field does negative work.

5. External work to move the charge slowly (no change of kinetic energy): $W_{\text{ext}} = -W_{AB} = \Delta E_p = q(V_B - V_A)$.6. Check the sign physically: a positive charge released in a field accelerates along $\vec{E}$ and loses potential energy; a negative charge accelerates opposite to $\vec{E}$.**WARNING** Sign Conventions — Classic GCE Traps

- $W_{\text{field}} = q\Delta V$ where $\Delta V = V_{\text{initial}} - V_{\text{final}}$. Do not confuse with $W_{\text{ext}} = q(V_{\text{final}} - V_{\text{initial}})$.
- An electron ($q = -e$) moving from the negative plate to the positive plate moves against $\vec{E}$ but along $\vec{F}$ (since $\vec{F} = -e\vec{E}$). The field does positive work, the electron gains kinetic energy.
- "Potential energy of the charge" means $E_p = qV$. It decreases when the field does positive work.

WORKED EXAMPLE 9 Moving a charge between charged plates

Two horizontal parallel plates are separated by $d = 5.0$ cm and maintained at a p.d. of $V = 200$ V, the upper plate being positive. An electron ($e = 1.60 \times 10^{-19}$ C, $m_e = 9.11 \times 10^{-31}$ kg) is moved slowly from the lower plate to the upper plate. (a) Find the electric field between the plates. (b) Calculate the work done by the electric force during this displacement. (c) Calculate the work that an external agent must supply. (d) If the electron is instead released from rest at the upper plate, find its speed on reaching the lower plate.

SOLUTION

(a) Field. For parallel plates,

$$E = \frac{V}{d} = \frac{200}{5.0 \times 10^{-2}} = 4.0 \times 10^3 \text{ V m}^{-1}$$

directed downwards (from the + plate to the - plate).

(b) Work of the electric force. The electron carries $q = -e$, so the electric force on it points upwards (opposite to $\vec{E}$). The displacement is also upwards, so the field does positive

work:

$$W = |q| E d = (1.60 \times 10^{-19})(4.0 \times 10^3)(5.0 \times 10^{-2}) = 3.2e - 17 \text{ J.}$$

Equivalently, $W = |q|V = e \times 200 \text{ V} = 3.2e - 17 \text{ J}$ — a useful shortcut: the work only depends on the p.d. crossed, not on the path.

(c) External work. Moving the electron slowly means $\Delta E_k = 0$, so

$$W_{\text{ext}} = -W = -3.2e - 17 \text{ J.}$$

The external agent actually holds back the electron; the field does the pushing.

(d) Released from the upper plate. The electron is negative, the force on it is upwards, so released at the upper plate it accelerates upwards — it cannot reach the lower plate. The intended physical situation is release from the lower plate. Then energy conservation gives

$$\frac{1}{2}m_e v^2 = eV \Rightarrow v = \sqrt{\frac{2eV}{m_e}} = \sqrt{\frac{2(1.60 \times 10^{-19})(200)}{9.11 \times 10^{-31}}} = 8.4e6 \text{ m s}^{-1}.$$

Lesson: always check the sign of the charge before deciding the direction of motion.

7.2 Skill 2 — Torque on an electric dipole

DEFINITION Electric Dipole Moment

An **electric dipole** consists of two equal and opposite charges $+q$ and $-q$ separated by a distance d . Its **dipole moment** is the vector

$$\vec{p} = q \vec{d}$$

where $\vec{d}$ points from $-q$ to $+q$. Unit: C m.

PROPERTY Dipole in a Uniform Electric Field

- Net force: $\vec{F}_{\text{net}} = \vec{0}$ (forces $+q\vec{E}$ and $-q\vec{E}$ cancel).
- Torque (couple): $\vec{\tau} = \vec{p} \wedge \vec{E}$, magnitude $\tau = pE \sin \theta$, where θ is the angle between $\vec{p}$ and $\vec{E}$. The torque tends to align $\vec{p}$ with $\vec{E}$.
- Potential energy: $U = -\vec{p} \cdot \vec{E} = -pE \cos \theta$. Stable equilibrium at $\theta = 0$ ($U_{\text{min}} = -pE$); unstable at $\theta = 180^\circ$ ($U_{\text{max}} = +pE$).
- Work done by an external agent rotating the dipole from θ_1 to θ_2 (slowly):

$$W_{\text{ext}} = \Delta U = pE(\cos \theta_1 - \cos \theta_2).$$

Examinable: Derivation of $\tau = pE \sin \theta$ from the couple of forces $F = qE$ with lever arm $d \sin \theta$.

METHOD Dipole in a uniform field

1. Identify the dipole: two charges $+q$ and $-q$ separated by a fixed distance d .
2. Compute the **electric dipole moment**: $p = qd$, directed from $-q$ to $+q$.
3. The net force is zero, but the forces form a couple. The torque magnitude is

$$\tau = pE \sin \theta$$

where θ is the angle between $\vec{p}$ and $\vec{E}$.

4. Stable equilibrium: $\theta = 0$ ($\vec{p}$ parallel to $\vec{E}$). Unstable equilibrium: $\theta = 180^\circ$.
5. Work done by an external agent rotating the dipole from θ_1 to θ_2 :

$$W = pE(\cos \theta_1 - \cos \theta_2).$$

WORKED EXAMPLE 10 Torque on a dipole

An electric dipole consists of charges $\pm 2.0 \text{ nC}$ separated by 4.0 mm . It is placed in a uniform field $E = 5.0 \times 10^4 \text{ V m}^{-1}$. (a) Calculate the maximum torque on the dipole. (b) Calculate the work needed to rotate it from stable equilibrium to $\theta = 60^\circ$.

SOLUTION

(a) Dipole moment: $p = qd = (2.0 \times 10^{-6})(4.0 \times 10^{-3}) = 8.0 \times 10^{-9} \text{ C m}$. Maximum torque occurs at $\theta = 90^\circ$:

$$\tau_{\max} = pE = (8.0 \times 10^{-9})(5.0 \times 10^4) = 4.0 \times 10^{-4} \text{ N m}.$$

(b) From $\theta_1 = 0$ to $\theta_2 = 60^\circ$:

$$W = pE(\cos 0 - \cos 60^\circ) = 4.0 \times 10^{-4} (1 - 0.5) = 2.0 \times 10^{-4} \text{ J}.$$

The work is positive: the field tends to align the dipole, so the external agent must do work against it.


7.3 Skill 3 — Capacitance, parallel-plate formula and permittivity

DEFINITION Capacitance

A **capacitor** is a device that stores electric charge and energy. It consists of two conductors (plates) carrying equal and opposite charges $\pm Q$. The **capacitance** C is defined as

$$C = \frac{Q}{V}$$

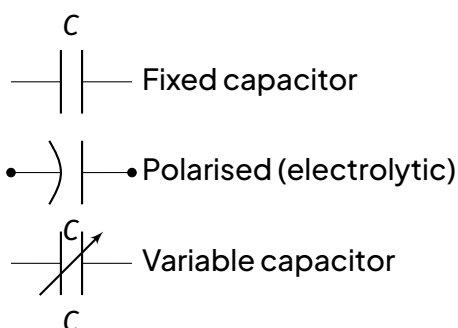where Q is the magnitude of the charge on one plate and V is the potential difference between the plates. Unit: the **farad** ($F = C V^{-1}$). Practical submultiples: μF (10^{-6}), nF (10^{-9}), pF (10^{-12}).



Standard circuit symbols for capacitors (IEC / European style).

KEY POINTS Types of Capacitors (Identification)

- Ceramic / Film: Non-polarised, small values (pF – μF), high frequency, low losses.
- Electrolytic (Aluminium/Tantalum): Polarised (marked $+/-$), large values (μF – F), used for smoothing/filtering. Must be connected with correct polarity.
- Variable: Air-spaced or plastic dielectric, capacitance adjusted by rotating plates (old radio tuners).

PROPERTY Parallel-Plate Capacitor Formula

For two parallel plates of area A (overlap area), separation d , with a dielectric of relative permittivity ϵ_r filling the gap:

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

where $\epsilon_0 = 8.85 \times 10^{-12} F m^{-1}$ (permittivity of free space). $\epsilon_r \geq 1$ (dimensionless); $\epsilon_r \approx 1$

for air/vacuum. Factors affecting C : $C \propto A$, $C \propto 1/d$, $C \propto \epsilon_r$. Examinable derivation:
 $E = \sigma/(\epsilon_0 \epsilon_r) = Q/(\epsilon_0 \epsilon_r A)$, $V = Ed = Qd/(\epsilon_0 \epsilon_r A) \Rightarrow C = Q/V = \epsilon_0 \epsilon_r A/d$.

METHOD Computing and measuring capacitance

1. Definition: $C = \frac{Q}{V}$, with Q the charge on one plate and V the p.d. between the plates.

2. Parallel-plate formula:

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

A : area of overlap of the plates; d : separation; $\epsilon_0 = 8.85 \times 10^{-12} \text{ F m}^{-1}$; ϵ_r : relative permittivity of the dielectric.

3. Factors affecting C : C increases with area A , decreases with separation d , and is multiplied by ϵ_r when a dielectric fills the gap.

4. Measurement: Charge the capacitor to a known p.d. V , then discharge it through a ballistic galvanometer (or measure Q with a coulombmeter); $C = Q/V$. Alternatively, use the discharge curve through a known resistor (Skill 7).

5. Insertion of a dielectric:

- At constant V (battery connected): $C \rightarrow \epsilon_r C$, $Q \rightarrow \epsilon_r Q$, $U \rightarrow \epsilon_r U$. Battery supplies energy.
- At constant Q (battery disconnected): $C \rightarrow \epsilon_r C$, $V \rightarrow V/\epsilon_r$, $U \rightarrow U/\epsilon_r$. Energy decreases (mechanical work done pulling dielectric in).

WARNING Dielectric Insertion — Constant V vs Constant Q

This is a classic GCE trap. Read the question carefully:

- "Battery remains connected" $\Rightarrow V$ constant $\Rightarrow Q$ and U increase by factor ϵ_r .
- "Battery disconnected before insertion" $\Rightarrow Q$ constant $\Rightarrow V$ and U decrease by factor ϵ_r .

The energy difference comes from the battery (constant V) or from mechanical work done by the field pulling the dielectric in (constant Q).

DID YOU KNOW? Relative Permittivity Values

Typical ϵ_r : Vacuum = 1 (exact), Air ≈ 1.0006 , Paper ≈ 3.5 , Mica $\approx 5-7$, Glass $\approx 5-10$, Water ≈ 80 , Barium Titanate ≈ 1200 . High- ϵ_r ceramics allow tiny SMD capacitors of several μF in your phone.

WORKED EXAMPLE 11 Parallel-plate capacitor with a dielectric

A parallel-plate capacitor has plates of area $A = 200 \text{ cm}^2$ separated by $d = 1.0 \text{ mm}$ of air ($\epsilon_r \approx 1$). (a) Calculate its capacitance. (b) It is connected to a 12 V battery; find the charge stored. (c) The battery remaining connected, a sheet of mica ($\epsilon_r = 6.0$) is inserted to fill the gap. Find the new capacitance, charge and energy stored. Comment.

SOLUTION

(a) Convert units: $A = 200 \times 10^{-4} \text{ m}^2 = 2.0e-2 \text{ m}^2$, $d = 1.0e-3 \text{ m}$.

$$C = \frac{\epsilon_0 A}{d} = \frac{(8.85e-12 \text{ F m}^{-1})(2.0e-2 \text{ m}^2)}{1.0e-3 \text{ m}} = 1.77e-10 \text{ F} \approx 177 \text{ pF}.$$

(b) $Q = CV = (1.77e-10 \text{ F})(12 \text{ V}) = 2.12e-9 \text{ C}$.

(c) With mica, $C' = \epsilon_r C = 6.0 \times 177 \text{ pF} = 1.06 \text{ nF}$. The battery stays connected, so $V = 12 \text{ V}$ is unchanged:

$$Q' = C'V = 6.0 Q = 1.27e-8 \text{ C}.$$

Energy: $U = \frac{1}{2}CV^2$ gives initially $U = \frac{1}{2}(1.77e-10 \text{ F})(12 \text{ V})^2 = 1.27e-8 \text{ J}$, and finally

$$U' = \frac{1}{2}C'V^2 = 6.0 U = 7.6e-8 \text{ J}.$$

Comment: at fixed V , both Q and U are multiplied by ϵ_r . The extra energy is supplied by the battery (half of the battery's work goes into the capacitor, half into mechanical work pulling the dielectric in). Had the battery been disconnected first, Q would be fixed and the energy would decrease by a factor ϵ_r — a classic GCE trap.

7.4 Skill 4 — Capacitors in series and in parallel

PROPERTY Combination Rules

- Parallel: Same p.d. V across each. Charges add: $Q_{\text{tot}} = Q_1 + Q_2 + \dots$

$$C_{\text{eq}} = C_1 + C_2 + \dots \quad (\text{adds, like resistors in series})$$

- Series: Same charge Q on each (connected end-to-end, no other path). Voltages

add: $V = V_1 + V_2 + \dots$ with $V_i = Q/C_i$.

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots \quad (\text{like resistors in parallel})$$

For two capacitors in series: $C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$.

- Voltage division in series: $V_1 = \frac{C_{\text{eq}}}{C_1} V = \frac{C_2}{C_1 + C_2} V$. The smallest capacitor takes the largest voltage.

METHOD Reducing combinations of capacitors

1. Identify the topology: capacitors are in **series** if they carry the same charge (connected end-to-end, no node between them); in **parallel** if they share the same p.d. (connected between the same two nodes).
2. Reduce step by step: start from the branch furthest from the source, replace series/parallel groups by their equivalent, until a single C_{eq} remains.
3. Work back: find total charge $Q_{\text{tot}} = C_{\text{eq}} V_{\text{supply}}$, then distribute charges and voltages through the network using the rules above.
4. Check: Kirchhoff's voltage law (sum of V around any loop = 0) and charge conservation at nodes.

WORKED EXAMPLE 12 Mixed network

Three capacitors $C_1 = 2 \text{ } \mu\text{F}$, $C_2 = 4 \text{ } \mu\text{F}$ and $C_3 = 12 \text{ } \mu\text{F}$ are connected as follows: C_2 and C_3 in parallel, the combination in series with C_1 , across a 24 V d.c. supply. Find (a) the equivalent capacitance, (b) the charge on each capacitor, (c) the p.d. across each capacitor.

SOLUTION

(a) Parallel branch: $C_{23} = C_2 + C_3 = 4 + 12 = 16 \text{ } \mu\text{F}$. Series with C_1 :

$$C_{\text{eq}} = \frac{C_1 C_{23}}{C_1 + C_{23}} = \frac{2 \times 16}{2 + 16} = \frac{32}{18} = 1.78 \text{ } \mu\text{F}.$$

(b) Charge drawn from the supply: $Q = C_{\text{eq}} V = (1.78 \times 10^{-6} \text{ F})(24 \text{ V}) = 4.27 \times 10^{-5} \text{ C} = 42.7 \text{ } \mu\text{C}$. Series elements carry the same charge: $Q_1 = Q_{23} = 42.7 \text{ } \mu\text{C}$. The p.d. across the parallel branch: $V_{23} = Q_{23}/C_{23} = 42.7/16 = 2.67 \text{ V}$. Hence $Q_2 = C_2 V_{23} = 4 \times 2.67 = 10.7 \text{ } \mu\text{C}$ and $Q_3 = C_3 V_{23} = 12 \times 2.67 = 32.0 \text{ } \mu\text{C}$. Check: $Q_2 + Q_3 = 42.7 \text{ } \mu\text{C} = Q_1$. ✓

(c) $V_1 = Q_1/C_1 = 42.7/2 = 21.3 \text{ V}$; $V_2 = V_3 = 2.67 \text{ V}$. Check: $V_1 + V_{23} = 21.3 + 2.67 = 24 \text{ V}$. ✓ Reflex: always finish with Kirchhoff checks — they cost ten seconds and catch most errors.

7.5 Skill 5 — Energy stored in capacitors

PROPERTY Energy Stored in a Charged Capacitor

Three equivalent forms — choose the one matching the given data:

$$U = \frac{1}{2}QV = \frac{1}{2}CV^2 = \frac{Q^2}{2C}.$$

Examinable derivation: During charging, the work to add charge dq against the existing p.d. $v = q/C$ is $dW = v dq$; integrating from 0 to Q :

$$U = \int_0^Q \frac{q}{C} dq = \frac{Q^2}{2C}.$$

For combinations: compute the energy of each capacitor with its own Q_i and V_i , then add — or use $U = \frac{1}{2}C_{\text{eq}}V_{\text{total}}^2$. Both must agree.

WARNING Energy is NOT Conserved in Charge Sharing

When capacitors are reconnected (e.g. a charged capacitor joined to an uncharged one), charge is conserved but energy is not — the difference is dissipated as heat in the connecting wires (and radiation/spark). Never write "energy conserved" in such problems.

WORKED EXAMPLE 13 Energy before and after sharing charge

A $C_1 = 4 \text{ } \mu\text{F}$ capacitor is charged to 100 V then disconnected from the supply. It is then connected across an uncharged $C_2 = 8 \text{ } \mu\text{F}$ capacitor. Find (a) the initial energy, (b) the common p.d. after connection, (c) the final total energy, (d) the energy dissipated.

SOLUTION

(a) Initial charge: $Q = C_1 V_1 = (4 \text{ } \mu\text{F})(100 \text{ V}) = 400 \text{ } \mu\text{C}$.

$$U_i = \frac{1}{2}C_1 V_1^2 = \frac{1}{2}(4 \text{ } \mu\text{F})(100 \text{ V})^2 = 2.0 \text{ } \mu\text{J} = 20 \text{ mJ}.$$

(b) After connection the capacitors are in parallel; total charge is conserved and the p.d.

V' is common:


$$V' = \frac{Q}{C_1 + C_2} = \frac{400 \text{ } \mu\text{C}}{12 \text{ } \mu\text{F}} = 33.3 \text{ V}.$$

(c) $U_f = \frac{1}{2}(C_1 + C_2)V'^2 = \frac{1}{2}(12 \text{ } \mu\text{F})(33.3 \text{ V})^2 = 6.67 \text{ } \mu\text{J} = 6.7 \text{ mJ}$. (d) Energy dissipated:

$$\Delta U = U_i - U_f = 20 - 6.7 = 13.3 \text{ mJ},$$

lost as heat in the wires (and a spark if the leads touch!). Notice that two-thirds of the energy vanished even though no charge was lost — energy is not conserved in this process.

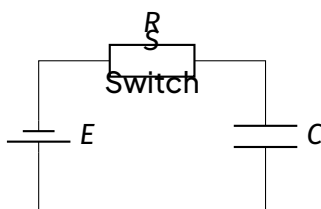7.6 Skill 6 — Charging a capacitor through a resistor



Series RC charging circuit. Switch closes at $t = 0$.

PROPERTY RC Charging Equations

Circuit: battery of e.m.f. E , switch, resistor R , capacitor C in series. Capacitor initially uncharged ($q(0) = 0$). Kirchhoff's loop law: $E = Ri + \frac{q}{C}$, with $i = \frac{dq}{dt}$. Differential equation:

$\frac{dq}{dt} + \frac{q}{RC} = \frac{E}{R}$. Solution (with $q(0) = 0$):

$$q(t) = Q_0(1 - e^{-t/\tau}), \quad Q_0 = CE, \quad \tau = RC.$$

Hence

$$u_C(t) = E(1 - e^{-t/\tau}), \quad i(t) = \frac{E}{R}e^{-t/\tau}.$$

Limits:

- At $t = 0$: $q = 0$, $u_C = 0$, $i = E/R$ (capacitor behaves like a wire / short circuit).
- As $t \rightarrow \infty$: $q \rightarrow CE$, $u_C \rightarrow E$, $i \rightarrow 0$ (capacitor behaves like an open switch).

Time constant $\tau = RC$: after $t = \tau$, $q = 0.63 Q_0$; after $t = 5\tau$ the charge exceeds 99% of Q_0 — the capacitor is taken as fully charged.

METHOD RC charging: setting up and using the equations

1. Draw the circuit, label E , R , C , switch. Define current direction (usually from + of battery).
2. Write Kirchhoff's loop equation: $E = Ri + q/C$.
3. Substitute $i = dq/dt$ to get the differential equation.
4. Write the standard solution $q(t) = CE(1 - e^{-t/RC})$ and derive $u_C(t)$, $i(t)$.
5. Identify $\tau = RC$. Compute numerical values.
6. Interpret $t = 0$ and $t \rightarrow \infty$ behaviour (short circuit / open circuit).

WORKED EXAMPLE 14 Charging a capacitor

A $100\ \mu\text{F}$ capacitor, initially uncharged, is charged through a $47\ \text{k}\Omega$ resistor from a $12\ \text{V}$ supply. (a) Calculate the time constant. (b) Write the equations for $u_C(t)$ and $i(t)$. (c) Find u_C and i at $t = 0$ and at $t = \tau$. (d) After how long is the capacitor 99% charged?

SOLUTION

(a) $\tau = RC = (47 \times 10^3)(100 \times 10^{-6}) = 4.7\ \text{s}$.

(b) $Q_0 = CE = (100 \times 10^{-6})(12\ \text{V}) = 1.2 \times 10^{-3}\ \text{C}$, and $I_0 = E/R = 12\ \text{V}/47 \times 10^3 = 2.55 \times 10^{-4}\ \text{A}$.

$$u_C(t) = 12\ \text{V}(1 - e^{-t/4.7}), \quad i(t) = 2.55 \times 10^{-4}\ \text{A} e^{-t/4.7}.$$


(c) At $t = 0$: $u_C = 0$ and $i = I_0 = 0.255\ \text{mA}$ — all the e.m.f. appears across R . At $t = \tau = 4.7\ \text{s}$: $u_C = 12(1 - e^{-1}) = 12(0.632) = 7.6\ \text{V}$; $i = I_0 e^{-1} = 0.255 \times 0.368 = 0.094\ \text{mA}$.

(d) We need $1 - e^{-t/\tau} = 0.99$, i.e. $e^{-t/\tau} = 0.01$, so

$$t = \tau \ln 100 = 4.7 \times 4.605 = 21.6\ \text{s} \quad (\approx 4.6\tau).$$

Interpretation: charging is fast at first (large current, empty capacitor opposing nothing) and slows down as u_C approaches E and opposes the battery.

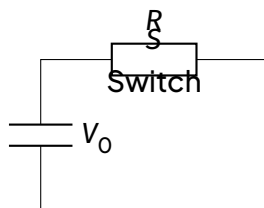7.7 Skill 7 — Discharging a capacitor through a resistor



Series RC discharging circuit. Capacitor pre-charged to V_0 , switch closes at $t = 0$ (battery removed).

PROPERTY RC Discharging Equations

Set-up: the charged capacitor ($Q_0 = CV_0$) is connected across R (supply removed). Loop law: $Ri + \frac{q}{C} = 0$. Differential equation: $\frac{dq}{dt} = -\frac{q}{RC}$, giving

$$q(t) = Q_0 e^{-t/\tau}, \quad u_C(t) = V_0 e^{-t/\tau}, \quad i(t) = -\frac{V_0}{R} e^{-t/\tau}, \quad \tau = RC.$$

Limits: at $t = 0$, $u_C = V_0$ and $|i| = V_0/R$ (maximum); as $t \rightarrow \infty$, everything $\rightarrow 0$. After $t = \tau$, $u_C = 0.37 V_0$. Log-linear analysis (measuring C): $\ln u_C = \ln V_0 - \frac{t}{RC}$. Plotting $\ln u_C$ against t gives a straight line of gradient $-\frac{1}{RC}$; knowing R , one obtains C .

METHOD RC discharge and measuring C

1. Write the loop equation for the discharge loop (no battery): $Ri + q/C = 0$.
2. Substitute $i = dq/dt$ (current leaves the positive plate, so $i = -dq/dt$ if q is charge on positive plate; the equation becomes $dq/dt = -q/RC$).
3. Solution: $q = Q_0 e^{-t/RC}$, $u_C = V_0 e^{-t/RC}$, $|i| = (V_0/R) e^{-t/RC}$.
4. For experimental determination of C : measure u_C at various t , plot $\ln u_C$ vs t , gradient $m = -1/RC \Rightarrow C = -1/(mR)$.

WORKED EXAMPLE 15 Discharge curve and determination of C

A capacitor charged to $V_0 = 9.0 \text{ V}$ is discharged through a resistor $R = 220 \text{ k}\Omega$. A data logger records u_C : at $t = 10 \text{ s}$, $u_C = 3.3 \text{ V}$. (a) Show that the decay is consistent with an expo-

nential and estimate τ . (b) Deduce the capacitance. (c) Find the initial discharge current and the time at which it has fallen to 10% of that value.

SOLUTION

(a) For an exponential, $u_C = V_0 e^{-t/\tau}$, so

$$\tau = \frac{t}{\ln(V_0/u_C)} = \frac{10}{\ln(9.0/3.3)} = \frac{10}{\ln 2.727} = \frac{10}{1.003} \approx 10.0 \text{ s.}$$

(b) $C = \frac{\tau}{R} = \frac{10.0}{220 \times 10^3} = 4.55 \times 10^{-5} \text{ F} = 45.5 \text{ } \mu\text{F}$.

(c) Initial current: $I_0 = V_0/R = 9.0/(220 \times 10^3) = 4.09 \times 10^{-5} \text{ A} = 41 \text{ } \mu\text{A}$. Current falls to 10% when $e^{-t/\tau} = 0.10$:


$$t = \tau \ln 10 = 10.0 \times 2.303 = 23.0 \text{ s.}$$

Check by energy: the energy initially stored, $\frac{1}{2}CV_0^2 = \frac{1}{2}(45.5 \times 10^{-6} \text{ F})(81 \text{ V}^2) = 1.84 \text{ mJ}$, is entirely dissipated in R during the discharge.

7.8 Skill 8 — Full analysis of a charge/discharge problem (GCE synthesis)

METHOD Tackling a two-way switch problem

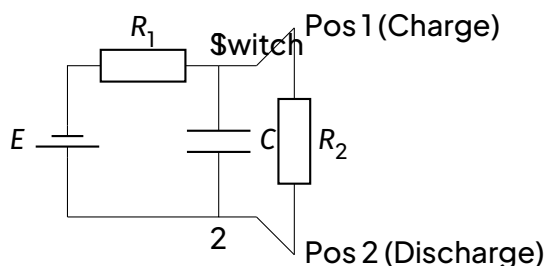1. Identify the two switch positions: position 1 = charging (battery in circuit), position 2 = discharging (battery excluded).
2. Write the initial condition for each phase: the charge on C (and hence u_C) is continuous — it cannot jump instantaneously.
3. Apply the charging or discharging solution with the correct τ (the resistance in the loop during that phase).
4. Sketch $u_C(t)$: exponential rise towards E (charge), exponential fall towards 0 (discharge).
5. Answer energy questions with $U = \frac{1}{2}Cu_C^2$ evaluated at the instants asked.



Two-way switch: Position 1 charges C through R_1 from battery E ; Position 2 discharges C through R_2 .

WORKED EXAMPLE 16 Charge then discharge

A two-way switch connects in position 1 a battery ($E = 6.0 \text{ V}$), a resistor $R_1 = 10 \text{ k}\Omega$ and a capacitor $C = 220 \text{ }\mu\text{F}$ in series. The capacitor is initially uncharged. (a) The switch is put in position 1 for 5.0 s . Find u_C at the end of this phase. (b) The switch is then flipped to position 2, connecting C across $R_2 = 4.7 \text{ k}\Omega$ only. Find u_C a further 2.0 s later. (c) Sketch qualitatively $u_C(t)$ for the whole experiment.

SOLUTION

(a) Charging phase. $\tau_1 = R_1 C = (10 \times 10^3)(220 \times 10^{-6}) = 2.2 \text{ s}$. After $t_1 = 5.0 \text{ s}$:

$$u_C = E(1 - e^{-t_1/\tau_1}) = 6.0(1 - e^{-5.0/2.2}) = 6.0(1 - 0.103) = 5.38 \text{ V} \approx 5.4 \text{ V}.$$

(b) Discharging phase. The capacitor starts this phase at $u_C(0) = 5.38 \text{ V}$ (charge is continuous). New time constant:

$$\tau_2 = R_2 C = (4.7 \times 10^3)(220 \times 10^{-6}) = 1.034 \text{ s}.$$

After a further $t_2 = 2.0 \text{ s}$:

$$u_C = 5.38 e^{-t_2/\tau_2} = 5.38 e^{-2.0/1.034} = 5.38 \times 0.1445 = 0.778 \text{ V} \approx 0.78 \text{ V}.$$

(c) Sketch: from 0 to 5 s , a concave-down exponential rise from 0 towards 6 V , reaching 5.4 V ; from 5 s onwards, a steeper exponential decay ($\tau_2 < \tau_1$) from 5.4 V towards 0, passing through 0.78 V at $t = 7 \text{ s}$. The slope is discontinuous at $t = 5 \text{ s}$ because the current changes abruptly, while u_C itself is continuous.

DID YOU KNOW? Applications in Cameroon

- Power factor correction: ENEC installs large capacitor banks (often $100 \text{ }\mu\text{F}$ to 1 mF , 400 V) near industrial motors to reduce reactive power and lower electricity bills.

- Camera flash / Phone flash: A battery charges a capacitor slowly ($\tau \sim \text{s}$) through a high resistance; the capacitor then discharges in $\sim 1 \text{ ms}$ through a xenon tube (very low R) giving a huge current ($\sim 100 \text{ A}$) for a bright flash.
- Defibrillators: Capacitors charged to $\sim 5000 \text{ V}$ store $\sim 300 \text{ J}$, discharged through paddles in $\sim 5 \text{ ms}$ to reset heart rhythm.

8 EXERCISES**8.1 I check my knowledge****EXERCISE 7 Multiple choice questions**

For each question, choose the single correct answer and justify your choice in one sentence.

1. The capacitance of a parallel-plate capacitor is doubled when:
 - (a) the p.d. across the plates is doubled;
 - (b) the charge on the plates is doubled;
 - (c) the plate separation is halved;
 - (d) the plate area is halved.
2. Two capacitors of capacitances $2\ \mu\text{F}$ and $4\ \mu\text{F}$ are connected in series. Their equivalent capacitance is:
 - (a) $6\ \mu\text{F}$;
 - (b) $3\ \mu\text{F}$;
 - (c) $1.33\ \mu\text{F}$;
 - (d) $0.75\ \mu\text{F}$.
3. The time constant of a circuit containing a resistor $R = 100\ \text{k}\Omega$ and a capacitor $C = 10\ \mu\text{F}$ is:
 - (a) $0.1\ \text{s}$;
 - (b) $1.0\ \text{s}$;
 - (c) $10\ \text{s}$;
 - (d) $1000\ \text{s}$.
4. When a capacitor discharges through a resistor, after a time $t = \tau$ the p.d. across it has fallen to approximately:
 - (a) 50 % of its initial value;
 - (b) 63 % of its initial value;
 - (c) 37 % of its initial value;
 - (d) zero.

EXERCISE 8 True or false? Justify

State whether each statement is true or false, and justify your answer with a law, a formula or a short argument.

1. The work done in moving a charge between two points in an electric field depends on the path followed.
2. The torque on an electric dipole in a uniform field is maximum when the dipole is perpendicular to the field.
3. Inserting a dielectric of relative permittivity ϵ_r between the plates of an isolated charged capacitor increases the p.d. across it.
4. In a series combination of capacitors, each capacitor carries the same charge.
5. The energy stored in a capacitor is $\frac{1}{2}CV^2$, so doubling the p.d. doubles the stored energy.

EXERCISE 9 Definitions and units

1. Define the **capacitance** of a capacitor and state its SI unit, expressing the farad in terms of the coulomb and the volt.
2. Define the **relative permittivity** ϵ_r of a dielectric. Why does ϵ_r have no unit?
3. Define the **time constant** τ of an RC circuit and give two physical interpretations of its value during the discharge of a capacitor.
4. State what is meant by the **electric dipole moment** $\vec{p}$ of a pair of charges $+q$ and $-q$ separated by a distance d , giving its magnitude, direction and SI unit.

EXERCISE 10 Quick calculations

1. A capacitor stores a charge of $60 \mu\text{C}$ when the p.d. across it is 12 V . Calculate its capacitance.
2. Calculate the energy stored in a $100 \mu\text{F}$ capacitor charged to 50 V .
3. A parallel-plate capacitor has plate area $A = 100 \text{ cm}^2$ and separation $d = 2.0 \text{ mm}$, with air between the plates ($\epsilon_0 = 8.85 \times 10^{-12} \text{ F m}^{-1}$). Calculate its capacitance.
4. A capacitor of $47 \mu\text{F}$ discharges through a $220 \text{ k}\Omega$ resistor. Calculate the time constant and the time taken for the p.d. to fall to 5 % of its initial value (take $\ln 20 \approx 3.0$).

8.2 I practise

EXERCISE 11 The electric dipole in a uniform field

An electric dipole consists of charges $+2.0 \mu\text{C}$ and $-2.0 \mu\text{C}$ separated by 2.0 mm . It is placed in a uniform electric field of strength $E = 5.0 \times 10^4 \text{ N C}^{-1}$, with its axis making an angle of 30° with the field direction.

1. Calculate the dipole moment p .
2. Calculate the torque Γ acting on the dipole.
3. Sketch the dipole in the field, showing the forces on each charge, and state the effect of the torque on the orientation of the dipole.
4. Identify the two equilibrium orientations of the dipole and state, with a reason, which one is stable.

EXERCISE 12 Parallel-plate capacitor with a dielectric

A parallel-plate capacitor has plate area $A = 200 \text{ cm}^2$ and plate separation $d = 1.0 \text{ mm}$. The space between the plates is completely filled with mica of relative permittivity $\epsilon_r = 6$. Take $\epsilon_0 = 8.85 \times 10^{-12} \text{ F m}^{-1}$.

1. Calculate the capacitance of the capacitor.
2. The capacitor is connected to a 100 V d.c. supply. Calculate the charge stored and the energy stored.
3. The capacitor is disconnected from the supply (so that its charge is trapped) and the mica sheet is then removed. Calculate the new capacitance and the new p.d. between the plates.
4. Explain why the p.d. changes, and calculate the change in stored energy. Suggest where this extra energy comes from.

EXERCISE 13 Series and parallel combinations

A $2 \mu\text{F}$ capacitor and a $4 \mu\text{F}$ capacitor are connected to a 12 V d.c. supply.

1. The capacitors are connected in series. Calculate (i) the equivalent capacitance, (ii) the charge on each capacitor, (iii) the p.d. across each capacitor, (iv) the total energy stored.
2. The same two capacitors are now connected in parallel across the same supply. Calculate the same four quantities.

3. Comment on the differences between the two arrangements, stating which combination stores more energy and why.

EXERCISE 14 Charging a capacitor through a resistor

A $100\ \mu\text{F}$ capacitor, initially uncharged, is charged through a $47\ \text{k}\Omega$ resistor from a $9.0\ \text{V}$ battery of negligible internal resistance.

1. Calculate the time constant of the circuit.
2. Write down the equation giving the charge $q(t)$ on the capacitor during charging, and calculate the charge at $t = \tau$.
3. Calculate the initial charging current (at $t = 0$) and the current at $t = 2\tau$.
4. Sketch, on the same axes, the curves of capacitor p.d. $V_C(t)$ and current $I(t)$ during the charging, indicating the values at $t = 0$, $t = \tau$ and as $t \rightarrow \infty$.
5. How long does it take for the capacitor to reach 99 % of its final charge? (Take $\ln 100 \approx 4.6$.)

8.3 I prepare for the GCE

EXERCISE 15 GCE-style structured question: combinations and energy

Two capacitors, $C_1 = 2\ \mu\text{F}$ and $C_2 = 4\ \mu\text{F}$, are available in the laboratory, together with a $12\ \text{V}$ d.c. supply, connecting leads and a two-way switch.

1. Define the capacitance of a capacitor and state its SI unit. (2 marks)
2. The capacitors are connected in series across the supply.
 - (a) Draw the circuit diagram. (1 mark)
 - (b) Calculate the equivalent capacitance of the combination. (2 marks)
 - (c) Calculate the charge on each capacitor and the p.d. across each. (3 marks)
 - (d) Calculate the total energy stored. (2 marks)
3. The capacitors are now connected in parallel across the same supply. Calculate the equivalent capacitance, the charge on each capacitor and the total energy stored. (4 marks)
4. Explain, in terms of charge distribution, why the p.d. is the same across each capacitor in parallel but the charge is shared in proportion to capacitance. (2 marks)

5. A student claims: “the series combination stores more energy because the charges add up”. Comment critically on this statement, using your results. (2 marks)

(Total: 18 marks)

EXERCISE 16 GCE-style data analysis: discharge of a capacitor

In an experiment to measure the capacitance of a capacitor, a charged capacitor is discharged through a resistor of resistance $R = 470 \text{ k}\Omega$. The p.d. V across the capacitor is measured at 10 s intervals, giving the following results:

t / s	0	10	20	30	40	50	60
V / V	12.0	7.3	4.4	2.7	1.6	1.0	0.6

1. State the equation describing the discharge of a capacitor through a resistor, defining each symbol. (2 marks)
2. Show that a graph of $\ln V$ against t should be a straight line, and state what its gradient and intercept represent. (3 marks)
3. Complete a table of values of $\ln(V/V_0)$ and plot the graph of $\ln V$ against t on graph paper, choosing suitable scales. (4 marks)
4. Use your graph to determine the time constant τ of the circuit, and hence calculate the capacitance C of the capacitor. (4 marks)
5. The resistor is stated by the manufacturer to have a tolerance of $\pm 5\%$, and the gradient is determined to within $\pm 4\%$. Estimate the percentage uncertainty in your value of C , and state the result in the form $C = (\dots \pm \dots) \mu\text{F}$. (3 marks)
6. Suggest one practical precaution that would improve the accuracy of the experiment. (1 mark)

(Total: 17 marks)

EXERCISE 17 GCE-style problem: flash lamp and energy transfer

Part A. A camera flash unit uses a capacitor of capacitance $2000 \mu\text{F}$ charged to 300 V . The flash is produced by discharging the capacitor through the flash lamp, and the useful flash duration is approximately equal to one time constant, $\tau = 1.0 \text{ ms}$.

1. Calculate the charge and the energy stored in the fully charged capacitor. (3 marks)

2. Estimate the resistance of the flash lamp during the discharge. (2 marks)
3. Calculate the initial discharge current, and explain why the brightness of the flash decreases with time. (3 marks)
4. Calculate the fraction of the initial energy still stored in the capacitor after one time constant. Comment on the efficiency of the flash. (3 marks)

Part B (extension). In a separate experiment, a $10\ \mu\text{F}$ capacitor is charged to 24 V , then disconnected from the supply and connected across an identical, initially uncharged $10\ \mu\text{F}$ capacitor.

5. Explain why charge is conserved in this process, and calculate the final p.d. across the combination. (3 marks)
6. Calculate the total energy stored before and after the connection, and show that energy appears to be “lost”. (3 marks)
7. Explain carefully where the “missing” energy has gone, naming at least two mechanisms. (2 marks)

(Total: 19 marks)

9 SOLUTIONS TO THE EXERCISES

10 CORRIGÉS DES EXERCICES — CHAPITRE PHY05 : CONDENSATEURS

SOLUTION Exercice 1 — Questions à choix multiples

- Bonne réponse : (c) la distance entre les armatures est divisée par deux.
Justification : pour un condensateur plan $C = \frac{\epsilon_0 \epsilon_r A}{d}$; la capacité ne dépend que de la géométrie et du diélectrique, pas de Q ni de V . Diviser d par deux double C ; diviser A par deux divise C par deux.
- Bonne réponse : (c) $1,33 \mu\text{F}$.
Justification : en série, $\frac{1}{C_s} = \frac{1}{2} + \frac{1}{4} = \frac{3}{4} \mu\text{F}^{-1}$, donc $C_s = \frac{4}{3} = 1,33 \mu\text{F}$. (Une association série est toujours plus petite que la plus petite capacité.)
- Bonne réponse : (b) $1,0 \text{ s}$.
Justification : $\tau = RC = (100 \times 10^3)(10 \times 10^{-6}) = 1,0 \text{ s}$.
- Bonne réponse : (c) 37% de sa valeur initiale.
Justification : $V = V_0 e^{-t/\tau}$; à $t = \tau$, $V = V_0 e^{-1} \approx 0,37 V_0$.

SOLUTION Exercice 2 — Vrai ou faux ? Justifier

- Faux. Le champ électrostatique est conservatif : le travail $W = q(V_B - V_A)$ ne dépend que des potentiels des extrémités, pas du chemin. C'est pourquoi le potentiel électrique est bien défini.
- Vrai. Le couple est $\Gamma = pE \sin \theta$; $\sin \theta$ est maximal ($= 1$) pour $\theta = 90^\circ$, c'est-à-dire quand l'axe du dipôle est perpendiculaire à $\vec{E}$.
- Faux. Pour un condensateur isolé, Q est constant. L'insertion du diélectrique multiplie C par ϵ_r , donc $V = Q/C$ est divisé par ϵ_r : la tension diminue. (Elle resterait constante seulement si le condensateur restait branché sur la source.)
- Vrai. En série, la charge déplacée dans le circuit est la même partout : les armatures intérieures portent $+Q$ et $-Q$ par induction, donc chaque condensateur porte la même charge Q .

5. Faux. $U = \frac{1}{2}CV^2$ varie comme le carré de la tension : doubler V multiplie l'énergie par 4, pas par 2.

SOLUTION Exercice 3 — Définitions et unités

1. La **capacité** C d'un condensateur est le rapport de la charge Q stockée sur une armature à la tension V entre les armatures : $C = \frac{Q}{V}$. Unité SI : le farad (F), avec $1\text{ F} = 1\text{ C V}^{-1}$ (un coulomb par volt).
2. La **permittivité relative** ϵ_r d'un diélectrique est le rapport de la capacité d'un condensateur rempli de ce diélectrique à la capacité du même condensateur sous vide : $\epsilon_r = \frac{C}{C_0} = \frac{\epsilon}{\epsilon_0}$. Étant un rapport de deux grandeurs de même nature (deux capacités ou deux permittivités), les unités se simplifient : ϵ_r est un nombre pur sans unité.
3. La **constante de temps** d'un circuit RC est $\tau = RC$. Interprétations en décharge : (i) c'est le temps après lequel la tension (ou la charge) est tombée à $e^{-1} \approx 37\%$ de sa valeur initiale ; (ii) c'est le temps que mettrait le condensateur pour se décharger complètement s'il continuait à se décharger à son taux initial (la tangente en $t = 0$ coupe l'axe des temps en $t = \tau$).
4. Le **moment dipolaire électrique** $\vec{p}$ de deux charges $+q$ et $-q$ séparées d'une distance d est le vecteur de norme $p = qd$, dirigé le long de l'axe du dipôle de la charge négative vers la charge positive. Unité SI : coulomb-mètre (C m).


SOLUTION Exercice 4 — Calculs rapides

1. $C = \frac{Q}{V} = \frac{60 \times 10^{-6}}{12} = 5,0 \times 10^{-6}\text{ F} = 5,0\text{ }\mu\text{F}$.
2. $U = \frac{1}{2}CV^2 = \frac{1}{2}(100 \times 10^{-6})(50)^2 = 0,125\text{ J} \approx 0,13\text{ J}$.
3. Conversion des unités : $A = 100\text{ cm}^2 = 1,0 \times 10^{-2}\text{ m}^2$, $d = 2,0 \times 10^{-3}\text{ m}$.

$$C = \frac{\epsilon_0 A}{d} = \frac{(8,85 \times 10^{-12})(1,0 \times 10^{-2})}{2,0 \times 10^{-3}} = 4,4 \times 10^{-11}\text{ F} = 44\text{ pF}.$$
4. $\tau = RC = (220 \times 10^3)(47 \times 10^{-6}) = 10,3\text{ s} \approx 10\text{ s}$.
 Pour $V = 0,05 V_0$: $0,05 = e^{-t/\tau} \Rightarrow t = \tau \ln 20 \approx 10,3 \times 3,0 \approx 31\text{ s}$.

SOLUTION Exercice 5 — Dipôle électrique dans un champ uniforme

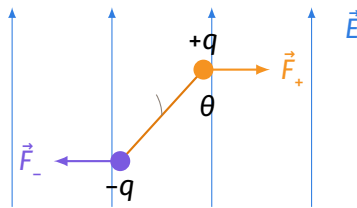1. $p = qd = (2,0 \times 10^{-6})(2,0 \times 10^{-3}) = 4,0 \times 10^{-9} \text{ C m}$.
2. $\Gamma = pE \sin \theta = (4,0 \times 10^{-9})(5,0 \times 10^4) \sin 30^\circ = (2,0 \times 10^{-4})(0,5) = 1,0 \times 10^{-4} \text{ N m}$.
3. Schéma : la force sur $+q$ est $\vec{F}_+ = q\vec{E}$ (parallèle à $\vec{E}$) ; la force sur $-q$ est $\vec{F}_- = -q\vec{E}$ (antiparallèle). Les deux forces sont égales et opposées mais non confondues : elles forment un couple.



Dipôle dans un champ uniforme : le couple $(\vec{F}_+, \vec{F}_-)$ produit un torque $\Gamma = pE \sin \theta$.

La force résultante est nulle (pas de translation), mais le couple fait tourner le dipôle pour aligner $\vec{p}$ avec $\vec{E}$ ($\theta \rightarrow 0$).

4. L'équilibre impose $\Gamma = 0$, soit $\theta = 0$ ou $\theta = 180^\circ$. $\theta = 0$ ($\vec{p}$ parallèle à $\vec{E}$) est l'équilibre stable : un petit déplacement produit un couple de rappel qui ramène le dipôle. $\theta = 180^\circ$ est instable : tout petit déplacement produit un couple qui l'éloigne (c'est aussi un maximum de l'énergie potentielle $U = -pE \cos \theta$).

SOLUTION Exercice 6 — Condensateur plan avec diélectrique

Données : $A = 200 \text{ cm}^2 = 2,0 \times 10^{-2} \text{ m}^2$; $d = 1,0 \times 10^{-3} \text{ m}$; $\epsilon_r = 6$.

1. $C = \frac{\epsilon_0 \epsilon_r A}{d} = \frac{(8,85 \times 10^{-12})(6)(2,0 \times 10^{-2})}{1,0 \times 10^{-3}} = 1,06 \times 10^{-9} \text{ F} \approx 1,1 \text{ nF}$.
2. $Q = CV = (1,06 \times 10^{-9})(100) = 1,06 \times 10^{-7} \text{ C} \approx 0,11 \mu\text{C}$.
 $U = \frac{1}{2} CV^2 = \frac{1}{2} (1,06 \times 10^{-9})(100)^2 = 5,3 \times 10^{-6} \text{ J} = 5,3 \mu\text{J}$.
3. Alimentation débranchée $\Rightarrow Q$ piégé : $Q = 1,06 \times 10^{-7} \text{ C}$ constant. Retrait de la mica divise la capacité par ϵ_r :

$$C' = \frac{C}{\epsilon_r} = \frac{1,06 \times 10^{-9}}{6} = 1,77 \times 10^{-10} \text{ F} \approx 0,18 \text{ nF}.$$

$$\text{Nouvelle tension : } V' = \frac{Q}{C'} = \epsilon_r V = 6 \times 100 = 600 \text{ V}.$$

4. La tension augmente car la même charge est stockée sur une capacité plus faible ($V = Q/C$). Nouvelle énergie :

$$U' = \frac{1}{2} C' V'^2 = \frac{1}{2} (1,77 \times 10^{-10}) (600)^2 = 3,2 \times 10^{-5} \text{ J} = 32 \mu\text{J}.$$

$\Delta U = U' - U \approx 27 \mu\text{J}$ (l'énergie est multipliée par $\epsilon_r = 6$). L'énergie supplémentaire provient du travail mécanique fourni par l'opérateur qui retire la plaque de mica : le diélectrique polarisé est attiré dans le champ, il faut donc fournir un travail contre cette attraction.

SOLUTION Exercice 7 — Associations série et parallèle

1. Série ($C_1 = 2 \mu\text{F}$, $C_2 = 4 \mu\text{F}$, $V = 12 \text{ V}$) :

(a) $\frac{1}{C_s} = \frac{1}{2} + \frac{1}{4} = \frac{3}{4} \Rightarrow C_s = \frac{4}{3} = 1,33 \mu\text{F}.$

(b) Même charge sur chacun : $Q = C_s V = (1,33 \times 10^{-6})(12) = 1,6 \times 10^{-5} \text{ C} = 16 \mu\text{C}.$

(c) $V_1 = \frac{Q}{C_1} = \frac{16}{2} = 8,0 \text{ V}$; $V_2 = \frac{Q}{C_2} = \frac{16}{4} = 4,0 \text{ V}.$ (Vérification : $V_1 + V_2 = 12 \text{ V}.$)

(d) $U_s = \frac{1}{2} C_s V^2 = \frac{1}{2} (1,33 \times 10^{-6})(144) = 9,6 \times 10^{-5} \text{ J} = 96 \mu\text{J}.$

2. Parallèle : même tension $V = 12 \text{ V}$ aux bornes de chacun.

(a) $C_p = C_1 + C_2 = 6,0 \mu\text{F}.$

(b) $Q_1 = C_1 V = 24 \mu\text{C}$; $Q_2 = C_2 V = 48 \mu\text{C}$ (total $72 \mu\text{C}$).

(c) $V_1 = V_2 = 12 \text{ V}.$

(d) $U_p = \frac{1}{2} C_p V^2 = \frac{1}{2} (6,0 \times 10^{-6})(144) = 4,3 \times 10^{-4} \text{ J} = 432 \mu\text{J}.$

3. L'association parallèle stocke plus d'énergie ($432 \mu\text{J} \gg 96 \mu\text{J}$) : les deux condensateurs sont chargés à la tension d'alimentation, donc la charge totale prélevée ($72 \mu\text{C}$) est bien plus grande qu'en série ($16 \mu\text{C}$), et $U = \frac{1}{2} QV$ est d'autant plus grande. En série la capacité équivalente est réduite en dessous de la plus petite valeur, ce qui limite la charge et l'énergie stockées.

SOLUTION Exercice 8 — Charge d'un condensateur à travers une résistance


1. $\tau = RC = (47 \times 10^3)(100 \times 10^{-6}) = 4,7 \text{ s}.$

2. $q(t) = Q_0 (1 - e^{-t/\tau})$ avec $Q_0 = CE = (100 \times 10^{-6})(9,0) = 9,0 \times 10^{-4} \text{ C}.$

À $t = \tau$: $q = Q_0(1 - e^{-1}) = 0,63 Q_0 = 5,7 \times 10^{-4} \text{ C}$.

3. Courant initial : $I_0 = \frac{E}{R} = \frac{9,0}{47 \times 10^3} = 1,9 \times 10^{-4} \text{ A} \approx 0,19 \text{ mA}$.
 $I(t) = I_0 e^{-t/\tau}$; à $t = 2\tau$: $I = I_0 e^{-2} = 0,135 I_0 \approx 2,6 \times 10^{-5} \text{ A} \approx 26 \mu\text{A}$.

4. Schéma :

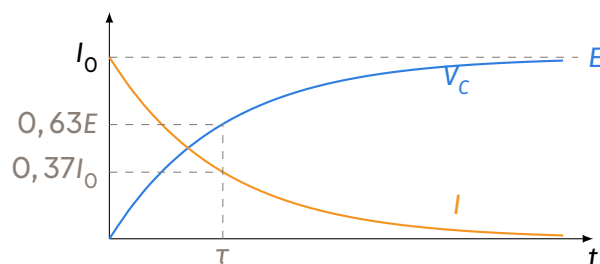

Charge : V_C monte vers E ; I décroît de $I_0 = E/R$ vers zéro. À $t = \tau$: $V_C = 0,63E$, $I = 0,37I_0$.


À $t = 0$: $V_C = 0$, $I = I_0$; quand $t \rightarrow \infty$: $V_C \rightarrow E = 9,0 \text{ V}$, $I \rightarrow 0$.

5. $q = 0,99 Q_0 \Rightarrow 1 - e^{-t/\tau} = 0,99 \Rightarrow e^{-t/\tau} = 0,01 \Rightarrow t = \tau \ln 100 = 4,7 \times 4,6 \approx 22 \text{ s}$.

SOLUTION

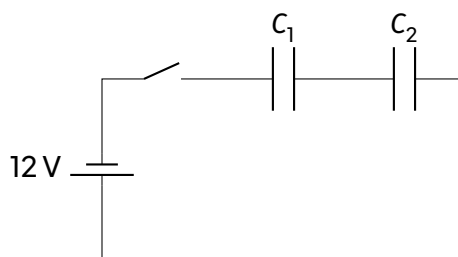Exercice 9 — Question de type GCE : associations et énergie

- (2 points) Capacité $C = Q/V$: charge stockée par unité de tension entre les armatures (1). Unité SI : le farad (F), $1 \text{ F} = 1 \text{ C V}^{-1}$ (1).
- Série :
 - (1 point) Schéma : source, interrupteur et les deux condensateurs en série dans une seule maille.



C_1 et C_2 en série aux bornes de la source 12 V.

- (b) (2 points) $\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{2} + \frac{1}{4} = \frac{3}{4} \mu\text{F}^{-1}$ (1) ; $C_s = 1,33 \mu\text{F}$ (1).
- (c) (3 points) $Q = C_s V = 1,33 \times 12 = 16 \mu\text{C}$ sur chaque condensateur (1) ; $V_1 = Q/C_1 = 8,0 \text{ V}$ (1) ; $V_2 = Q/C_2 = 4,0 \text{ V}$ (1).
- (d) (2 points) $U = \frac{1}{2} C_s V^2 = \frac{1}{2} (1,33 \times 10^{-6}) (12)^2$ (1) = $9,6 \times 10^{-5} \text{ J}$ (1).
3. Parallèle (4 points) : $C_p = 2 + 4 = 6,0 \mu\text{F}$ (1) ; $Q_1 = C_1 V = 24 \mu\text{C}$ (1) ; $Q_2 = C_2 V = 48 \mu\text{C}$ (1) ; $U = \frac{1}{2} C_p V^2 = 4,3 \times 10^{-4} \text{ J}$ (1).
4. (2 points) En parallèle, les deux paires d'armatures sont reliées directement aux deux mêmes bornes de la source, donc la tension aux bornes de chacune doit être égale à la tension de la source (1). Comme $Q = CV$ avec le même V , la charge prélevée est proportionnelle à la capacité : le condensateur le plus grand stocke proportionnellement plus de charge (1).
5. (2 points) L'affirmation est fausse. En série les charges ne s'additionnent pas : chaque condensateur porte la même charge $16 \mu\text{C}$, et l'énergie totale n'est que $96 \mu\text{J}$, contre $432 \mu\text{J}$ en parallèle (1). L'association parallèle stocke plus d'énergie car les deux condensateurs sont à la pleine tension 12 V et la charge totale stockée ($72 \mu\text{C}$) est bien plus grande (1).

Attentes du correcteur : utilisation correcte de la formule des inverses avec étapes montrées ; énoncé clair que la charge série est commune ; réponses numériques avec unités ; commentaire critique appuyé sur les propres résultats du candidat.

SOLUTION Exercice 10 — Question de type GCE : analyse de données (décharge)


1. (2 points) $V = V_0 e^{-t/\tau}$ avec $\tau = RC$ (1) ; V = tension à l'instant t , V_0 = tension initiale, R = résistance, C = capacité (1).
2. (3 points) En prenant les logarithmes népériens : $\ln V = \ln V_0 - \frac{t}{RC}$ (1), qui est de la forme

$y = c + mx$: une droite de pente $-\frac{1}{RC} = -\frac{1}{\tau}$ (1) et d'ordonnée à l'origine $\ln V_0$ (1).

3. (4 points) Tableau de valeurs :

t / s	0	10	20	30	40	50	60
V / V	12,0	7,3	4,4	2,7	1,6	1,0	0,6
$\ln(V/V)$	2,48	1,99	1,48	0,99	0,47	0,00	-0,51

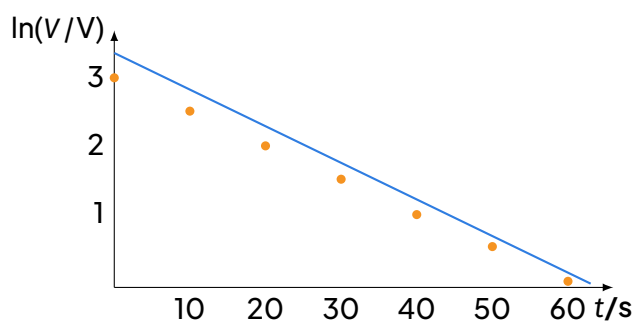Échelles : par ex. 2 cm : 10 s sur l'axe t et 2 cm : 0,5 unité sur l'axe $\ln V$. Tracer les points et tracer la droite de meilleur ajustement (1 point pour le tableau, 1 pour échelles/axes, 1 pour points, 1 pour droite).



$\ln V$ en fonction de t : droite de pente $-1/\tau$.

4. (4 points) Pente lue sur la droite : par ex. en utilisant (0, 2,48) et (60 s, -0,51) :

$$\text{pente} = \frac{-0,51 - 2,48}{60 - 0} = -5,0 \times 10^{-2} \text{ s}^{-1} \text{ (2 points pour grand triangle et valeur).}$$

$$\tau = -\frac{1}{\text{pente}} = \frac{1}{0,050} = 20 \text{ s (1).}$$

$$C = \frac{\tau}{R} = \frac{20}{470 \times 10^3} = 4,3 \times 10^{-5} \text{ F} = 43 \mu\text{F (1).}$$

5. (3 points) Comme $C = \tau/R$ et τ vient de la pente, les incertitudes relatives s'additionnent :

$$\frac{\Delta C}{C} = 4\% + 5\% = 9\% (1); \quad \Delta C = 0,09 \times 43 \approx 4 \mu\text{F (1);}$$

$$C = (43 \pm 4) \mu\text{F (1).}$$

6. (1 point) N'importe laquelle : utiliser un voltmètre à haute impédance (numérique) pour ne pas décharger le condensateur ; prendre des mesures à intervalles plus courts / plus de points ; répéter et faire la moyenne ; utiliser un enregistreur de données (data logger) pour acquérir V et t simultanément ; s'assurer que le condensateur est complètement chargé avant de commencer.

Attentes du correcteur : linéarisation explicitée ; valeurs des logs données à 2–3 chiffres significatifs ; pente lue sur un grand triangle de la droite de meilleur ajustement (pas sur les points bruts) ; incertitudes additionnées pour un quotient ; réponse finale avec précision cohérente.

SOLUTION Exercice 11 — Problème de type GCE : lampe flash et transfert d'énergie

Partie A.

- (3 points) $Q = CV = (2000 \times 10^{-6})(300) = 0,60 \text{ C (1)}$; $U = \frac{1}{2}CV^2 = \frac{1}{2}(2000 \times 10^{-6})(300)^2$ (1) = 90 J (1).
- (2 points) $\tau = RC \Rightarrow R = \frac{\tau}{C} = \frac{1,0 \times 10^{-3}}{2000 \times 10^{-6}}$ (1) = 0,50 Ω (1).
- (3 points) $I_0 = \frac{V}{R} = \frac{300}{0,50} = 600 \text{ A (1)}$. Pendant la décharge $V = V_0 e^{-t/\tau}$ et $I = I_0 e^{-t/\tau}$ décroissent exponentiellement (1) ; la puissance dissipée dans la lampe ($P = VI$) chute donc rapidement, ce qui fait diminuer la luminosité avec le temps (1).
- (3 points) Après $t = \tau$: $V = V_0 e^{-1}$, et comme $U \propto V^2$,

$$\frac{U}{U_0} = e^{-2} = 0,135 \approx 14\% (2).$$

Environ 86% de l'énergie stockée est restituée pendant le flash utile : le flash est assez efficace pour extraire l'énergie en une constante de temps (1).

Partie B.

- (3 points) Le système des deux condensateurs est isolé (débranché de la source), donc la charge totale est conservée : la charge se redistribue simplement entre les condensateurs jusqu'à ce qu'ils atteignent une tension commune (1). Charge initiale $Q = CV = (10 \mu\text{F})(24 \text{ V}) = 240 \mu\text{C}$. Tension commune finale :


$$V_f = \frac{Q}{C + C} = \frac{240 \mu\text{C}}{20 \mu\text{F}} = 12 \text{ V} (2).$$

- (3 points) Avant : $U_i = \frac{1}{2}(10 \times 10^{-6})(24)^2 = 2,88 \times 10^{-3} \text{ J} = 2,9 \text{ mJ (1)}$.
Après : $U_f = \frac{1}{2}(20 \times 10^{-6})(12)^2 = 1,44 \times 10^{-3} \text{ J} = 1,4 \text{ mJ (1)}$.
 $U_f = \frac{1}{2}U_i$: la moitié de l'énergie (1,44 mJ) a apparemment "disparu" (1).
- (2 points) L'énergie manquante est dissipée lors du passage du courant dans le circuit de connexion : (i) effet Joule dans la résistance des fils et des armatures (1) ; (ii) énergie rayonnée sous forme d'ondes électromagnétiques par l'étincelle/courant transitoire (et éventuellement son d'une étincelle) (1). L'énergie est globalement conservée ; elle n'est plus stockée dans les condensateurs.

Attentes du correcteur : distinction nette entre conservation de la charge (toujours)

et “perte” d’énergie (dissipation) ; utilisation correcte de $U \propto V^2$ pour la fraction e^{-2} ; mécanismes physiques plausibles cités pour l’énergie manquante.

11 SUMMARY SHEET

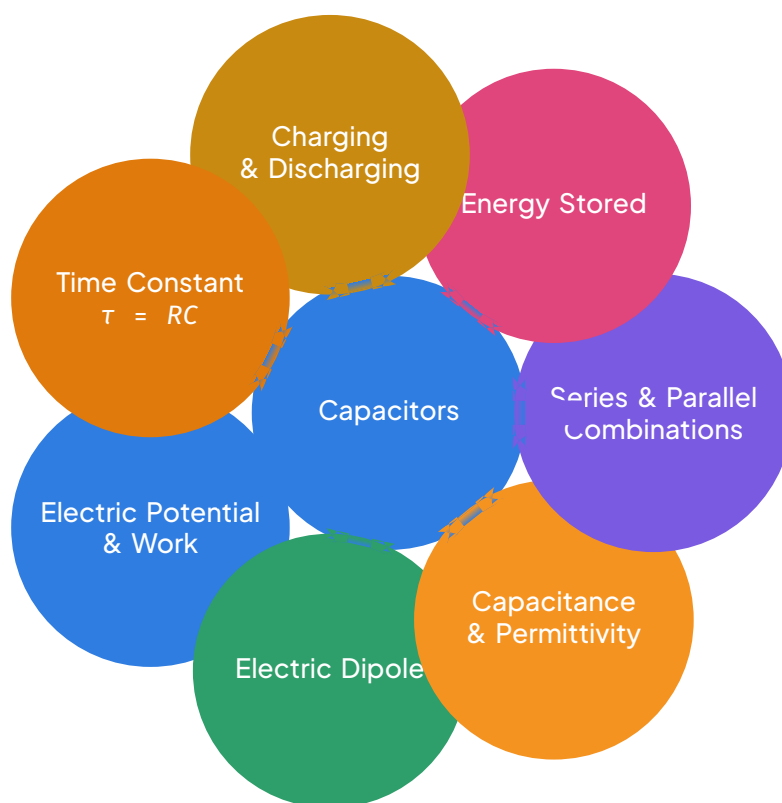

Mind map of Chapter PHY05: Capacitors

FICHE BILAN L'essentiel à connaître pour l'examen

Key Definitions

- **Electric potential** V at a point: work done per unit positive charge to bring it from infinity to that point. $V = \frac{W}{q}$, unit: volt (V) = J/C.
- **Potential difference** (p.d.) between two points: work done per unit charge moving between them. $V_{AB} = V_A - V_B = \frac{W_{AB}}{q}$.
- **Electric dipole**: two equal and opposite charges $\pm q$ separated by distance $2a$. Dipole moment $\vec{p} = q(2\vec{a})$, direction from $-q$ to $+q$.
- **Torque on a dipole** in uniform field $\vec{E}$: $\vec{\tau} = \vec{p} \times \vec{E}$, magnitude $\tau = pE \sin \theta$.
- **Capacitance** C of a conductor: ratio of charge Q to its potential V . $C = \frac{Q}{V}$, unit: farad (F) = C/V.

- **Parallel-plate capacitor:** $C = \frac{\epsilon_0 \epsilon_r A}{d}$ where $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$, ϵ_r = relative permittivity (dielectric constant), A = plate area, d = separation.
- **Time constant** $\tau = RC$ for an RC circuit: time for charge/current/voltage to change by factor $1/e$ ($\approx 37\%$) during discharge, or to reach $\approx 63\%$ of final value during charging.

Laws, Formulas & Theorems to Know

- Work done moving charge q through p.d. V : $W = qV$.
- Energy stored in a capacitor: $U = \frac{1}{2}QV = \frac{1}{2}CV^2 = \frac{Q^2}{2C}$.
- Capacitors in **parallel**: $C_{\text{eq}} = C_1 + C_2 + \dots$; same V , charges add.
- Capacitors in **series**: $\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$; same Q , voltages add.
- Charging a capacitor through resistor R from DC source V_0 :

$$\begin{aligned} Q(t) &= CV_0 (1 - e^{-t/RC}), \\ V_C(t) &= V_0 (1 - e^{-t/RC}), \\ I(t) &= \frac{V_0}{R} e^{-t/RC}. \end{aligned}$$

- Discharging a capacitor through resistor R :

$$\begin{aligned} Q(t) &= Q_0 e^{-t/RC}, \\ V_C(t) &= V_0 e^{-t/RC}, \\ I(t) &= -\frac{V_0}{R} e^{-t/RC} \quad (\text{magnitude } I_0 e^{-t/RC}). \end{aligned}$$

- At $t = 0$: capacitor acts as short circuit (uncharged) or open circuit (charged, no current). As $t \rightarrow \infty$: capacitor acts as open circuit (charged to V_0) or short circuit (discharged).
- Half-life for discharge: $t_{1/2} = \tau \ln 2 \approx 0.693 \tau$.

Methods

1. Finding equivalent capacitance: Identify series/parallel groups, reduce step by step. Redraw circuit after each reduction.
2. Energy problems: Use $U = \frac{1}{2}CV^2$ when V known; $U = \frac{Q^2}{2C}$ when Q known. For combinations, compute total energy from equivalent C and total V (or Q), or sum individual energies.
3. RC transient analysis: Write Kirchhoff's loop equation $\rightarrow$ differential equation $\rightarrow$ solve with initial condition. Memorise the standard exponential forms above.

4. Graph interpretation: Plot $\ln I$ vs t (discharge) $\rightarrow$ straight line slope $= -1/RC$. Plot $\ln(V_0 - V_C)$ vs t (charging) $\rightarrow$ slope $= -1/RC$.
5. Experimental determination of C : Use reed switch (charge/discharge at frequency f , measure average current $I = CVf$) or RC time constant method (measure τ with known R).

Common Mistakes

- Confusing series/parallel formulas: remember capacitors add in parallel (like resistors in series) and reciprocals add in series.
- Forgetting that Q is the same on all capacitors in series, but V splits; in parallel V is same, Q splits.
- Using $U = QV$ instead of $\frac{1}{2}QV$ for capacitor energy.
- Mixing up charging/discharging equations: check $t = 0$ and $t \rightarrow \infty$ limits.
- Ignoring the minus sign in discharge current (direction opposite to charging).
- Using $\tau = 1/RC$ instead of $\tau = RC$; dimensional check: $\Omega \cdot F = s$.
- Forgetting to convert μF , nF , pF to farads before calculation.
- In dipole torque, using $\cos \theta$ instead of $\sin \theta$; torque is maximum at $\theta = 90^\circ$.

GCE Tips

- Definitions are frequently asked verbatim (e.g. capacitance, farad, relative permittivity, time constant). Learn them precisely.
- Derivations: Be able to derive $C = \epsilon_0 A/d$ for parallel plates, energy $U = \frac{1}{2}CV^2$, and the charging/discharging equations from Kirchhoff's law.
- Graph work: Know how to linearise $I = I_0 e^{-t/RC}$ by plotting $\ln I$ vs t . The slope gives $-1/RC$. Label axes with units.
- Numerical questions: Always show the formula, substitution with units, and final answer with unit. Use $g = 9.81$ or 10 as instructed. Keep 3 significant figures unless told otherwise.
- Practical: Describe the reed switch method or the RC circuit with a stop-watch/voltmeter. Mention safety (discharge capacitor before handling).
- Multiple choice: Watch for distractors with wrong units (e.g. $\tau = R/C$), wrong exponential form, or confusion between Q , V , I at $t = 0$ and $t = \infty$.
- Structured questions: Often combine topics: e.g. a dipole in a uniform field created by a capacitor; or energy loss when connecting charged capacitors (charge redistributes, energy not conserved due to radiation/heat).



Signed • OnBuch+
ONBUCH+ TEACHING TEAM
FOLLOWS THE OFFICIAL MINESEC SYLLABUS

OnBuch+